

Online Examinations (Even Sem/Part-I/Part-II Examinations 2020 - 2021)

Course Name - Basic Electronics II: Analog Electronics

Course Code - EC201

* You can submit the form ONLY ONCE.

* Fill the following information for further process.

* Required

1. Email *

2. Name of the Student *

3. Enter Full Student Code *

4. Enter Roll No *

5. Enter Registration No *

6. Enter Course Code *

7. Enter Course Name *

8. *

Mark only one oval.

- Diploma in Pharmacy
- Bachelor of Pharmacy
- B.TECH.(CSE)
- B.TECH.(ECE)
- BCA
- B.SC.(CS)
- B.SC.(BT)
- B.SC.(ANCS)
- B.SC.(HN)
- B.Sc.(MM)
- B.A.(MW)
- BBA
- [B.COM](#)
- B.A.(JMC)
- BBA(HM)
- BBA(LLB)
- B.OPTOMETRY
- B.SC.(MB)
- B.SC.(MLT)
- B.SC.(MRIT)
- B.SC.(PA)
- LLB
- [B.SC\(IT\)-AI](#)
- B.SC.(MSJ)
- Bachelor of Physiotherapy
- B.SC.(AM)
- Dip.CSE
- Dip.ECE
- [DIP.EE](#)
- DIP.CE

- [DIP.ME](#)
- PGDHM
- MBA
- M.SC.(BT)
- M.TECH(CSE)
- LLM
- M.A.(JMC)
- M.A.(ENG)
- M.SC.(MATH)
- M.SC.(MB)
- MCA
- M.SC.(MSJ)
- M.SC.(AM)
- M.SC.CS)
- M.SC.(ANCS)
- M.SC.(MM)
- B.A.(Eng)

Answer all the questions. Each question carry one mark.

9. 1. An ideal OP AMP has

Mark only one oval.

- infinite input impedance
- zero output impedance
- infinite voltage gain
- all of the these

10. 2. The feedback element in the integrator is a

Mark only one oval.

- capacitor
- inductor
- diode
- resistance

11. 3. The common mode rejection ratio of an OP AMP is

Mark only one oval.

- much smaller than unity
- much larger than unity
- unity
- none of these

12. 4. With zero volts on both inputs, an OP-amp ideally should have an output

Mark only one oval.

- equal to the positive supply voltage
- equal to the negative supply voltage
- equal to zero
- equal to CMRR

13. 5. The use of negative feedback

Mark only one oval.

- reduces the voltage gain of an Op-amp
- makes the Op-amp oscillate
- makes linear operation possible
- both reduces the voltage gain of an Op-amp & makes the Op-amp oscillate

14. 6. A voltage follower

Mark only one oval.

- has a voltage gain of 1
- is non-inverting
- has no feedback resistor
- All of these

15. 7. A FET operates on

Mark only one oval.

- Majority carriers only
- Minority carriers
- Positive and negative ions
- Positively charged ions

16. 8. A FET is better chopper than a BJT because it has

Mark only one oval.

- Low offset voltage
- High input voltage
- High input current
- High series ON resistance

17. 9. How to improve CMRR value

Mark only one oval.

- Increase common mode gain
- Decrease common mode gain
- Increase Differential mode gain
- Decrease differential mode gain

18. 10. In which of the following configuration does a MOSFET works as an amplifier?

Mark only one oval.

- ommon Source (CS)
- Common Gate (CG)
- Common drain (CD)
- All of these

19. 11. The transistor operates in saturation region if

Mark only one oval.

- Collector junction is reverse biased and the emitter junction is forward biased
- Collector junction is forward biased and the emitter junction is reverse biased
- Both the collector junction and the emitter junction are forward biased
- Both the collector junction and the emitter junction are reverse biased

20. 12. Which of the following is not an example for non-sinusoidal oscillator?

Mark only one oval.

- Sawtooth Generators
- Blocking oscillators
- Multivibrator
- Crystal oscillators

21. 13. Which of the following oscillator is not using a feedback network for its oscillation?

Mark only one oval.

- LC oscillator
- RC oscillator
- Crystal oscillator
- Relaxation oscillators

22. 14. The operating point is also called the

Mark only one oval.

- Cut off point
- Quiescent point
- Saturation point
- None of these

23. 15. The voltage follower is commonly used as

Mark only one oval.

- Switch
- Isolator
- Regulator
- None of these

24. 16. A quartz crystal oscillator consists of

Mark only one oval.

- Only series resonant frequency
- Only parallel resonant frequency
- Both series and parallel frequencies
- Neither series nor parallel frequency

25. 17. The resonant frequency of a Wien-bridge oscillator is around

Mark only one oval.

- 10 Hz
- 10 KHz
- 100 KHz
- 10MHz

26. 18. The voltage gain of single-stage CE amplifier increases with

Mark only one oval.

- Increase in ac load resistance
- Decrease in ac load resistance
- Increase in source resistance
- Increase r_e

27. 19. The phase shift oscillator requires an external phase shift of

Mark only one oval.

- 90°
- 180°
- 270°
- 360°

28. 20. If the input to the ideal comparator is a sinusoidal signal of 8 V (peak to peak) without any DC component, then the output of the comparator has a duty cycle of

Mark only one oval.

- 1/2
- 1/6
- 1/3
- 1/12

29. 21. If an amplifier with a gain of -1000 and feedback factor $\beta = -0.1$ had a gain change of 20% due to temperature, the change in the gain of the feedback amplifier would be

Mark only one oval.

- 10%
- 5%
- 0.2%
- 0.01%

30. 22. The maximum efficiency of a Class B push-pull amplifier is

Mark only one oval.

- 78.5%
- 50%
- 33%
- 48.5%

31. 23. Which one of the following is correct?

Mark only one oval.

$h_{fe} = \alpha$

$h_{fe} = \beta$

$h_{fe} = -\alpha$

$h_{fe} = -\beta$

32. 24. An operational amplifier possesses

Mark only one oval.

Very large input resistance and very large output resistance

Very large input resistance and very small output resistance

Very small input resistance and very small output resistance

Very small input resistance and very large output resistance

33. 25. An operational amplifier has an open-loop gain of 200,000. Its output exhibits saturation at 10V. The threshold differential voltage of the amplifier is

Mark only one oval.

25 micro V

50 micro-V

0.5 mili-V

10 V

34. 26. If the differential voltage gain and the common mode voltage gain of a differential amplifier are 48dB and 2 dB respectively, then its common mode rejection ratio is

Mark only one oval.

- 23dB
- 25dB
- 46dB
- 50dB

35. 27. The output of a certain op-amp circuit changes by 20 V in 4 micro-sec. Its slew rate is

Mark only one oval.

- 50 V/micro-sec
- 500 V/micro-sec
- 5 V/micro-sec
- 5 mV/micro-sec

36. 28. Inverting op-amp is

Mark only one oval.

- Voltage shunt feedback
- Voltage series feedback
- Current series feedback
- Current shunt feedback

37. 29. In case of active integrator if the output voltage is larger than VCC, overall gain

Mark only one oval.

- Increase
- Decrease
- Remains constant
- None of these

38. 30. The zero level detector is one application of a

Mark only one oval.

- Differentiator
- Integrator
- Summing amplifier
- Comparator

39. 31. Which of the following are the non-linear applications of OP-AMP?

Mark only one oval.

- Current-to-voltage converter
- Comparator
- Peak detector
- Limiter

40. 32. Which transistor bias circuit provides good Q-point stability with a single-polarity supply voltage?

Mark only one oval.

- Base bias
- Collector-feedback bias
- Voltage-divider bias
- None of these

41. 33. Which of the following statements is true of phase-shift type and Wien-bridge-type RC oscillator?

Mark only one oval.

- Both use positive feedback.
- The phase-shift type oscillator uses positive feedback only whereas Wien-bridge oscillator uses both positive and negative feedback.
- The phase-shift-type oscillator uses both positive and negative feedback whereas the Wien-bridge oscillator uses positive feedback only
- Both use negative feedback

42. 34. The feedback element in a differentiator is a

Mark only one oval.

- Resistance
- Capacitor
- Inductor
- Diode

43. 35. The maximum rate of change of output voltage per unit time is

Mark only one oval.

- Slew rate
- CMRR
- Offset voltage
- None of these

44. 36. The slew rate of an ideal OP AMP is

Mark only one oval.

- 0
- infinity
- 10 V/micro-sec
- 1 V/micro-sec

45. 37. Which of the following electrical characteristics is not exhibited by an ideal op-amp?

Mark only one oval.

- Infinite voltage gain
- Infinite bandwidth
- Infinite output resistance
- Infinite slew rate

46. 38. Consider the inverting OP-AMP with R_1 (input resistance) = 1k-ohm, R_2 (feedback resistance) = 50k-ohm and power supply voltages $\pm 12V$. Find the output voltage for an input voltage 1V.

Mark only one oval.

- 50 V
- +50 V
- 12 V
- +12 V

47. 39. The Op-amp can amplify _____.

Mark only one oval.

- A.C. signals only
- D.C. signals only
- both A.C. and D.C. signals
- neither D.C. nor A.C. signals

48. 40. How many h-parameters are there for a transistor?

Mark only one oval.

- Four
- Two
- Five
- Three

49. 41. The dimensions of hie parameter are

Mark only one oval.

- Ohm
- Mho
- Farad
- None of these

50. 42. If the input is a rectangular pulse, the output of an integrator is

Mark only one oval.

- Sine wave
- Square wave
- Ramp wave
- Rectangular wave

51. 43. Current can not flow to ground through

Mark only one oval.

- A mechanical ground
- An AC ground
- A virtual ground
- An ordinary ground

52. 44. An ideal OP-AMP has bandwidth

Mark only one oval.

- Zero
- Small
- Large
- Infinite

53. 45. Voltage controlled oscillators are used commonly in

Mark only one oval.

- Pulse Modulators
- Frequency Modulators
- Phase Clocked loops
- All of these

54. 46. Every practical oscillator loop gain is

Mark only one oval.

- Less than unity
- Greater than unity
- Equal to unity
- None of these

55. 47. Oscillator actually does not generate energy but merely convert the energy available from

Mark only one oval.

- DC biasing source
- Active device
- Mechanical input
- None of these

56. 48. When temperature changes h parameters of a transistor

Mark only one oval.

- Also change
- Do not change
- May or may not change
- None of above

57. 49. An emitter follower has input impedance

Mark only one oval.

- Low
- High
- Zero
- None of these

58. 50. Which of the following is radio frequency oscillator?

Mark only one oval.

- phase shift oscillator
- Hartley oscillator
- Wein bridge oscillator
- None of these

59. 51. The oscillator follows

Mark only one oval.

- Nyquist criteria
- Barkhausen criteria
- Coulomb' law
- None of these

60. 52. The disadvantage of crystal oscillator is

Mark only one oval.

- Not availability of low frequency
- Not availability of high frequency around MHz
- Both
- none of these

61. 53. When a large sine wave drives a Schmitt trigger, the output is a

Mark only one oval.

- Rectangular wave
- Triangular wave
- Rectified sine wave
- Series of ramps

62. 54. For oscillation to start, the loop gain $A\beta$ of the oscillator must be

Mark only one oval.

- Infinitely high
- More than one
- Exactly one
- Less than one

63. 55. Crystals have a very

Mark only one oval.

- Low Q
- High Q
- Small inductance
- Large resistance

64. 56. Wein-bridge oscillator can typically generate frequencies in the range of

Mark only one oval.

- 1 kHz – 1 MHz
- 1 MHz – 10 MHz
- 10 MHz – 100 MHz
- 100 MHz – 150 MHz

65. 57. An oscillator of LC type that has a split capacitor in the circuit is

Mark only one oval.

- Hartley oscillator
- Colpitt oscillator
- Wein-bridge oscillator
- RC phase shift oscillator

66. 58. The advantages of negative feedback amplifier are

Mark only one oval.

- High input impedance
- Increase in gain stability
- Low output impedance
- All of these

67. 59. A certain OP-amp has input bias currents of 50 micro-A and 49.3 micro-A. The input offset current is

Mark only one oval.

- 700nA
 99.3 micro-A
 49.3 A
 None of these

68. 60. If a transistor is operated in such a way that output current flows for 160 degrees of the input signal, then it is _____ operation

Mark only one oval.

- Class A
 Class C
 Class B
 Class AB

69. 61. For MOSFET is to be used as a switch then it must operate in

Mark only one oval.

- Cut-off region
 Triode region
 Saturation region
 Both cut-off and triode region can be used

70. 62. Which of the following class have a theoretical efficiency of 50%?

Mark only one oval.

- Class A
- Class C
- Class AB
- Class B

71. 63. The band pass filter

Mark only one oval.

- transmit Frequencies between f_1 and f_2
- Blocks frequencies between f_1 and f_2
- Both a and b
- None of these

72. 64. The crystal oscillator frequency is very stable due to

Mark only one oval.

- Rigidity of crystal
- Size of crystal
- Structure of crystal
- High Q of the crystal

73. 65. 1 MHz sinusoidal signal can be obtained from

Mark only one oval.

- Hartley oscillator
- RC phase shift oscillator
- Wein bridge oscillator
- All of these

74. 66. The cut-off point on the dc load line is

Mark only one oval.

- $V_{CE}=V_{CC}, I_C = 0$
- $V_{BE}= V_{CC}, I_C=0$
- $V_{CE}=0, I_C= 0$
- $V_{BE}=0, I_B=0$

75. 67. An operational amplifier has an open-loop gain of 200,000. Its output exhibits saturation at 10V. The threshold differential voltage of the amplifier is

Mark only one oval.

- 25 micro Volts
- 50 micro Volts
- 0.5 mili Volts
- 10 Volts

76. 68. Inverting op-amp is

Mark only one oval.

- Voltage shunt feedback
- Voltage series feedback
- Current series feedback
- Current shunt feedback

77. 69. Which transistor bias circuit provides good Q-point stability with a single-polarity supply voltage?

Mark only one oval.

- Base bias
- Collector-feedback bias
- Voltage-divider bias
- None of these

78. 70. Operating point represents

Mark only one oval.

- Values of I_C and V_{CE} when signal is applied
- The magnitude of signal
- Zero signal values of I_C and V_{CE}
- none of these

This content is neither created nor endorsed by Google.

Google Forms