

Online Examinations (Even Sem/Part-I/Part-II Examinations 2020 - 2021)

Course Name - APPLIED & DIGITAL ELECTRONICS

Course Code -DEE404

* You can submit the form ONLY ONCE.

* Fill the following information for further process.

* Required

1. Email *

2. Name of the Student *

3. Enter Full Student Code *

4. Enter Roll No *

5. Enter Registration No *

6. Enter Course Code *

7. Enter Course Name *

8. *

Mark only one oval.

- Diploma in Pharmacy
- Bachelor of Pharmacy
- B.TECH.(CSE)
- B.TECH.(ECE)
- BCA
- B.SC.(CS)
- B.SC.(BT)
- B.SC.(ANCS)
- B.SC.(HN)
- B.Sc.(MM)
- B.A.(MW)
- BBA
- [B.COM](#)
- B.A.(JMC)
- BBA(HM)
- BBA(LLB)
- B.OPTOMETRY
- B.SC.(MB)
- B.SC.(MLT)
- B.SC.(MRIT)
- B.SC.(PA)
- LLB
- [B.SC\(IT\)-AI](#)
- B.SC.(MSJ)
- Bachelor of Physiotherapy
- B.SC.(AM)
- Dip.CSE
- Dip.ECE
- [DIP.EE](#)
- DIP.CE

- [DIP.ME](#)
- PGDHM
- MBA
- M.SC.(BT)
- M.TECH(CSE)
- LLM
- M.A.(JMC)
- M.A.(ENG)
- M.SC.(MATH)
- M.SC.(MB)
- MCA
- M.SC.(MSJ)
- M.SC.(AM)
- M.SC.CS)
- M.SC.(ANCS)
- M.SC.(MM)
- B.A.(Eng)

Answer all the questions. Each question carry one mark.

9. 1.Which type of triggering is shown by the D flip flops in buffer registers for the temporary storage of digital words?

Mark only one oval.

- Positive level triggering
- Negative level triggering
- Positive edge triggering
- Negative edge triggering

10. 2.The full form of TCTL is _____.

Mark only one oval.

- Transistor-coupled transistor logic
- Transistor-capacitor transistor logic
- Transistor-complemented transistor logic
- Transistor-complementary transistor logic

11. 3.On subtracting $(001100)_2$ from $(101001)_2$ using 2's complement, we get _____.

Mark only one oval.

- 1101100
- 11101
- 11010101
- 11010111

12. 4.The primary advantage of RTL technology was that

Mark only one oval.

- It results as low power dissipation
- It uses a minimum number of resistors
- It uses a minimum number of transistors
- It operates swiftly

13. 5.What is the addition of the binary numbers 11011011010 and 010100101?

Mark only one oval.

- 0111001000
- 1100110110
- 11101111111
- 10011010011

14. 6.An OR gate has 4 inputs. One input is high and the other three are low. The output is

Mark only one oval.

- alternately high and low
- High
- Low
- None of these

15. 7.In a sequential circuit, the output at any time depends only on the input values at that time.

Mark only one oval.

- Past output values
- Past output and Present input
- Intermediate values
- Present input values

16. 8.Reflected binary code is also known as _____.

Mark only one oval.

- BCD code
- Binary code
- ASCII code
- Gray Code

17. 9.There are many situations in logic design in which simplification of logic expression is possible in terms of XOR and _____ operations.

Mark only one oval.

- X-NOR
- X-OR
- NOR
- NAND

18. 10.What is the function of an enable input on a multiplexer chip?

Mark only one oval.

- To apply Vcc
- To connect ground
- To active the entire chip
- To active one half of the chip

19. 11.The number 140 in octal is equivalent to?

Mark only one oval.

(90)₁₀

(88)₁₀

(86)₁₀

(96)₁₀

20. 12.Which input values will cause an AND logic gate to produce a HIGH output?

Mark only one oval.

At least one input is HIGH

At least one input is LOW

All inputs are HIGH

All inputs are LOW

21. 13.Which of the following is the Universal Flip-flop?

Mark only one oval.

S-R flip-flop

J-K flip-flop

Master slave flip-flop

D Flip-flop

22. 14.The canonical sum of product form of the function $y(A,B) = A + B$ is

Mark only one oval.

$AB + BB + A'A$

$AB + AB' + A'B$

$BA + BA' + A'B'$

$AB' + A'B + A'B'$

23. 15.The expression for Absorption law is given by _____

Mark only one oval.

$A + AB = A$

$A + AB = B$

$AB + AA' = A$

$A + B = B + A$

24. 16.Two bit addition is done by _____.

Mark only one oval.

ripple carry adder

carry sum adder

full adder

half adder

25. 17. Don't care conditions can be used for simplifying Boolean expressions in _____.

Mark only one oval.

Registers

Terms

K-maps

Latches

26. 18. Which gates are ideal for checking the parity bits?

Mark only one oval.

AND

NAND

EX-OR

EX-NOR

27. 19. $(734)_8 = (?)_{16}$

Mark only one oval.

C1D

DC1

1CD

1DC

28. 20.1's complement can be easily obtained by using

Mark only one oval.

- Comparator
- Inverter
- Adder
- Subtractor

29. 21.Convert the hexadecimal number (1E2)₁₆ to decimal:

Mark only one oval.

- 480
- 498
- 482
- 484

30. 22.The logical sum of two or more logical product terms is called _____.

Mark only one oval.

- SOP
- POS
- OR operation
- NAND operation

31. 23.A demultiplexer is used to-

Mark only one oval.

- Route the data from single input to one of many outputs
- Perform serial to parallel conversion
- Both Route the data from single input to one of many outputs & Perform serial to parallel conversion
- Select data from several inputs and route it to single output

32. 24.The basic R-S flip-flop is

Mark only one oval.

- A monostable multivibrator
- A bistable multivibrator
- An astable multivibrator
- A Schmitt trigger

33. 25.Internal propagation delay of asynchronous counter is removed by _____

Mark only one oval.

- Ripple counter
- Ring counter
- Modulus counter
- Synchronous counter

34. 26. In the toggle mode a JK flip-flop has-

Mark only one oval.

J = 0, K = 0

J = 1, K = 1

J = 0, K = 1

J = 1, K = 0

35. 27. How many NOT gates are required to implement the Boolean expression: $X = AB'C + A'BC$?

Mark only one oval.

2

3

4

5

36. 28. Convert $(0.345)_{10}$ into an octal number:

Mark only one oval.

$(0.16050)_8$

$(0.26050)_8$

$(0.19450)_8$

$(0.24040)_8$

37. 29.TTL circuits with “totem-pole” output stage minimize

Mark only one oval.

- The power dissipation in RTL
- The time consumption in RTL
- The speed of transferring rate in RTL
- Propagation delay in RTL

38. 30.In a multiplexer, the selection of a particular input line is controlled by _____

Mark only one oval.

- Data controller
- Selected lines
- Logic gates
- Both data controller and selected lines

39. 31.The inverter can be produced with how many NAND gates?

Mark only one oval.

- 1
- 3
- 2
- 4

40. 32. In which operation, carry is obtained?

Mark only one oval.

- Subtraction
- Addition
- Multiplication
- Addition and Subtraction

41. 33. $(A + B)(A' * B') = ?$

Mark only one oval.

- 1
- 0
- AB
- AB'

42. 34. Standard TTL circuits operate with a __ volt power supply

Mark only one oval.

- 2
- 5
- 4
- 6

43. 35.The enable input is also known as _____

Mark only one oval.

- Select input
- Decoded input
- Strobe
- Sink

44. 36.The universal gate is _____.

Mark only one oval.

- NAND gate
- OR gate
- NOT gate
- AND gate

45. 37.How many NAND circuits are contained in a 7400 NAND IC?

Mark only one oval.

- 1
- 2
- 4
- 8

46. 38. Ripple counters are also called _____.

Mark only one oval.

- SSI counters
- Asynchronous counters
- Synchronous counters
- VLSI counters

47. 39. In Boolean algebra, the OR operation is performed by which properties

Mark only one oval.

- Associative properties
- Commutative properties
- Distributive properties
- All of these

48. 40. Simplify $Y = AB' + (A' + B)C$.

Mark only one oval.

- $AB' + C$
- $AB + AC$
- $A'B + AC'$
- $AB + A$

49. 41.How many AND gates are required for a 8-to-1 multiplexer?

Mark only one oval.

5

7

8

6

50. 42.The NOR gate output will be high if the two inputs are _____.

Mark only one oval.

0

1

10

11

51. 43.What is one disadvantage of an S-R flip-flop?

Mark only one oval.

It has no Enable input

It has a RACE condition

It has no clock input

Invalid State

52. 44.How many shift registers are used in a 4-bit serial adder?

Mark only one oval.

2

3

4

5

53. 45.The digit F in Hexadecimal system is equivalent to in decimal system.

Mark only one oval.

13

14

15

17

54. 46.In 1-to-4 demultiplexer, how many select lines are required?

Mark only one oval.

2

3

4

1

55. 47.The Boolean function $A + BC$ is a reduced form of _____.

Mark only one oval.

- $AB + BC$
- $(A + B)(A + C)$
- $A'B + AB'C$
- $(A + C)B$

56. 48.If A, B and C are the inputs of a full adder then the carry is given by _____

Mark only one oval.

- A AND B OR (A OR B) AND C
- A OR B OR (A AND B) C
- (A AND B) OR (A AND B)C
- A XOR B XOR (A XOR B) AND C

57. 49.When two 16-input multiplexers drive a 2-input MUX, what is the result?

Mark only one oval.

- 2-input MUX
- 4-input MUX
- 16-input MUX
- 32-input MUX

58. 50. Which of the following circuits come under the class of combinational logic circuits? 1. Full adder 2. Full subtractor 3. Half adder 4. J-K flip 5. Counter

Mark only one oval.

- 1 only
- 3 and 4
- 4 and 5
- 1, 2 and 3

59. 51. The decimal equivalent of the binary number $(1011.011)_2$ is _____.

Mark only one oval.

- $(11.375)_{10}$
- $(10.123)_{10}$
- $(11.175)_{10}$
- $(9.23)_{10}$

60. 52. If the number of n selected input lines is equal to 2^m then it requires _____ select lines.

Mark only one oval.

- 2
- m
- n
- $2n$

61. 53.The output of a subtractor is given by (if A, B and X are the inputs)_____

Mark only one oval.

- A AND B XOR X
- A XOR B XOR X
- A OR B NOR X
- A NOR B XOR X

62. 54.A disadvantage of DTL is

Mark only one oval.

- The input transistor to the resistor
- The input resistor to the transistor
- The increased fan-in
- The increased fan-out

63. 55.A combinational circuit that selects one from many inputs are _____

Mark only one oval.

- Encoder
- Decoder
- Demultiplexer
- Multiplexer

64. 56.EncoderDecoderDemultiplexerMultiplexer

Mark only one oval.

S = R = 0

S = 0, R = 1

S = 1, R = 0

S = R = 1

65. 57.TTL is called transistor–transistor logic because both the logic gating function and the amplifying function are performed by _____.

Mark only one oval.

Resistors

Bipolar junction transistors

One transistor

Resistors and transistors respectively

66. 58.The excess-3 code for 597 is given by _____.

Mark only one oval.

100011001010

100010100111

10110010111

10110101101

67. 59. Resistor–transistor logic (RTL) is a class of digital circuits built using _____ as the input network and _____ as switching devices.

Mark only one oval.

- Resistors, bipolar junction transistors (BJTs)
- Bipolar junction transistors (BJTs), Resistors
- Capacitors, resistors
- Resistors, capacitors

68. 60. Which of the following circuit can be used as parallel to serial converter?

Mark only one oval.

- Multiplexer
- Demultiplexer
- Decoder
- Digital counter

This content is neither created nor endorsed by Google.

Google Forms