

# Online Assessment (Even Sem/Part-I/Part-II Special Examinations of Intermediate semester 2019 - 2020)

Course Name - Electrical Technology

Course Code - DCSE/DECE206/DEE206/DME206/DCE206

\* You can submit the form ONLY ONCE.

\* Fill the following information for further process.

\* Required

1. Email address \*

---

2. Name of the Student \*

---

3. Enter Full Student Code \*

---

4. Enter Roll No \*

---

5. Enter Registration No \*

---

6. Enter Course Code \*

---

7. Enter Course Name \*

---

## 8. Select Your Programme \*

Mark only one oval.

- Diploma in Pharmacy
- Bachelor of Pharmacy
- B.TECH.(CSE)
- B.TECH.(ECE)
- BCA
- B.SC.(CS)
- B.SC.(BT)
- B.SC.(ANCS)
- B.SC.(HN)
- B.Sc.(MM)
- B.A.(MW)
- BBA
- [B.COM](#)
- B.A.(JMC)
- BBA(HM)
- BBA(LLB)
- B.OPTOMETRY
- B.SC.(MB)
- B.SC.(MLT)
- B.SC.(MRIT)
- B.SC.(PA)
- LLB
- PGDHM
- Dip.CSE
- Dip.ECE
- Dip.EE
- Dip.CE
- Dip.ME
- MCA
- M.SC.(CS)

- M.SC.(ANCS)
- M.SC.(MM)
- MBA
- M.SC.(BT)
- M.TECH(CSE)
- LLM
- M.A.(JMC)
- M.A.(ENG)
- M.SC.(MATH)
- M.SC.(MB)

Answer all the questions. Each question carry one mark.

9. 1. KVL can be applied at

*Mark only one oval.*

- Loop
- Node
- Both loop and node
- Neither loop nor node

10. 2. Unit of capacitance is

*Mark only one oval.*

- Mho
- Ohm
- Farad
- Henry

11. 3. How many coulombs of charge flow through a circuit carrying a current of 10 A in 1 minute?

*Mark only one oval.*

- 10
- 60
- 600
- 1200

12. 4. Delta connection is also known as \_\_\_\_\_

*Mark only one oval.*

- Y-connection
- Mesh connection
- Either Y-connection or mesh connection
- Neither Y-connection nor mesh connection

13. 5. Which of the following is not an expression power?

*Mark only one oval.*

- $P=VI$
- $P=I^2R$
- $P=V^2/R$
- $P=I/R$

14. 6. A 250V bulb passes a current of 0.1A. Calculate the power in the lamp.

*Mark only one oval.*

- 75 W
- 50 W
- 25 W
- 90 W

15. 7. The SI unit of power is?

*Mark only one oval.*

- kW(kilo-watt)
- J/s(joules per second)
- Ws(watt-second)
- J/h(joules per hour)

16. 8. The power factor of an Resonance R-L-C circuit is

*Mark only one oval.*

- often zero
- between zero and 1
- always unity
- between zero and -1

17. 9. The voltage applied across an R-L circuit is equal to \_\_\_ of  $V_R$  and  $V_L$  .

*Mark only one oval.*

- arithmetic sum
- algebraic sum
- phasor sum
- sum of the squares

18. 10. Quality factor-Q of a resonant circuit signifies:

*Mark only one oval.*

- Loss in the resonant circuit
- Gain in the resonant circuit
- Magnetic energy stored in the circuit
- Electric energy stored in the circuit

19. 11. At resonance, the circuit appears \_\_\_\_\_.

*Mark only one oval.*

- Inductive
- Capacitive
- Resistive
- Either inductive or capacitive

20. 12. The form factor is the ratio of

*Mark only one oval.*

- Peak value to r.m.s. value
- r.m.s. value to average value
- Average value to r.m.s. value
- None of these

21. 13. Fleming's right hand rule may be applied to

*Mark only one oval.*

- Motor
- Generator
- Transformer
- All of these

22. 14. For a coil having a magnetic circuit of constant reluctance, the flux is \_\_\_\_\_ to the current.

*Mark only one oval.*

- Directly proportional
- Inversely proportional
- Not related
- Very large compared to



23. 15. Identify which of the following is the unit of magnetic flux?

*Mark only one oval.*

- Weber
- Weber/m
- Tesla
- Weber-1

24. 16. A magnetic field exists around

*Mark only one oval.*

- iron
- copper
- aluminium
- moving charges

25. 17. Distributors fed at both ends has an advantage of \_\_\_\_\_.

*Mark only one oval.*

- continuous supply
- fault isolation
- being economical
- all of the mentioned

26. 18. The rated voltage of a 3 phase power system is given by

*Mark only one oval.*

- rms peak voltage
- rms line to line voltage
- Peak phase voltage
- Peak line to line voltage

27. 19. Full form of MCB

*Mark only one oval.*

- Miniature Circuit Breaker
- Mini Circuit Breaker
- Minimum Current Breaker
- Maximum Current Breaker

28. 20. A DC generator without commutator is a

*Mark only one oval.*

- AC generator
- DC motor
- DC generator
- induction motor

29. 21. The motor ratings are usually expressed in.....

*Mark only one oval.*

- Volts
- Amperes
- Kw
- KVA

30. 22. Turns ratio of the transformer is inversely proportional to \_\_\_\_\_

*Mark only one oval.*

- Resistance ratio
- Frequency ratio
- Current ratio
- Not proportional to any terms

31. 23. One telsa is equal to

*Mark only one oval.*

- 1 Wb/mm<sup>2</sup>
- 1 Wb/m
- 1 Wb/m<sup>2</sup>
- 1 mWb/m<sup>2</sup>

32. 24. Reciprocal of permeability is

*Mark only one oval.*

- reluctance
- permittivity
- susceptibility
- conductance

33. 25. In the left hand rule, forefinger always represents

*Mark only one oval.*

- voltage
- current
- magnetic field
- direction of force on the conductor

34. 26. Circuit breakers work

*Mark only one oval.*

- constantly
- only once
- when there is resistance
- when there is magnetic field

35. 27. The internal resistance of an ideal voltmeter will be

*Mark only one oval.*

- Infinity
- Zero
- Very small
- large

36. 28. The fuse rating is expressed in terms of

*Mark only one oval.*

- current
- voltage
- VAR
- kVA

37. 29. Full form of ELCB

*Mark only one oval.*

- Earth-leakage Circuit Breaker
- Earth-leak Circuit Breaker
- Earth-lag circuit Breaker
- Earth-lead Circuit Breaker

38. 30. The materials with permeability less than unity are called

*Mark only one oval.*

- Diamagnetic materials
- Paramagnetic materials
- Ferromagnetic materials
- Anti ferromagnetic materials

---

This content is neither created nor endorsed by Google.

Google Forms