



BRAINWARE UNIVERSITY

Course – BSc(HN)

Basic Electronics II: Analog Electronics (EC201/BHNG201)

(Semester – 2)

Time allotted: 3 Hours

Full Marks : 70

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group –A

(Multiple Choice Type Questions)

10 x 1 = 10

1. *Choose the correct alternative from the following*

(i) The common-mode gain is

- a. very high
- b. very low
- c. always unity
- d. unpredictable

(ii) A voltage follower

- a. has a voltage gain of 1
- b. is non-inverting
- c. has zero feedback resistor
- d. has all of these

(iii) Operating point represents

- a. values of i_c and v_{ce} when signal is applied
- b. the magnitude of signal voltage
- c. zero signal values of I_C and V_{CE}
- d. none of these

(iv) The input offset current equals the

- a. difference between two base currents
- b. average of two base currents
- c. collector current divided by current gain
- d. none of these

- (v) For proper operation of the transistor, its collector should have
- proper forward bias
 - proper reverse bias
 - very small size
 - none of the these
- (vi) An ideal value of stability factor is
- 100
 - 200
 - more than 200
 - 1
- (vii) Hartley oscillator is commonly used in
- radio receivers
 - radio transmitters
 - TV receivers
 - none of these
- (viii) The piezoelectric effect in a crystal is
- a voltage developed because of mechanical stress
 - a change in resistance because of temperature
 - a change in frequency because of temperature
 - none of these
- (ix) When voltage feedback (negative) is applied to an amplifier, its input impedance
- is decreased
 - is increased
 - remains the same
 - any one of these
- (x) A JFET has three terminals, namely
- cathode, anode, grid
 - source, gate, drain
 - emitter, base, collector
 - none of these

Group – B

(Short Answer Type Questions)

3 x 5 = 15

Answer any *three* from the following

- What is slew rate? Explain virtual ground concept of an Op-Amp. [2+3]
- What do you mean by CMRR of an Op-Amp? Calculate the common mode gain of an operational amplifier from the following parameters: the differential voltage gain $A_d=10^4$ and $CMRR=2000$. [2+3]
- Compare a FET with a BJT. Illustrate why BJT is called the current controlled device. [3+2]
- Describe the use of an OPAMP as a comparator. [5]
- Establish the relation $\mu = r_{dg_m}$, where the notations have their usual meanings. [5]

Group – C

(Long Answer Type Questions)

3 x 15 = 45

Answer any *three* from the following

7. (a) Draw the circuit diagram for the collector-to-base bias of an n-p-n transistor in the CE configuration. Obtain expressions for its stability factors. [7]
- (b) In the collector to base bias circuit of a transistor, $V_{CC}=12\text{ V}$, $R_B=100\text{ K}\Omega$ and $R_L=2\text{ K}\Omega$. If $\beta=99$, $I_{CO}=20\text{ nA}$ and $V_{BE}=0.7\text{ V}$, determine I_B , I_C and V_{CE} . Also find the stability factor w. r. t. I_{CO} . Here, notations used have their usual meanings. [8]
8. (a) Develop the theory of action of an OPAMP as a differentiator. [5]
- (b) Draw the circuit diagram of a difference amplifier using an OPAMP and find an expression for the output voltage. [2+5]
- Write short notes on input offset voltage. [3]
9. (a) Explain with a circuit diagram the action of a Wien bridge oscillator. Find an expression for the frequency of oscillation. [2+3]
- (b) Prove that the gain of the amplifier used in a Wien-bridge oscillator must be greater than 3 for sustained oscillations. [5]
- (c) A Wien-bridge oscillator has a frequency of 1000 Hz and a capacitance of 100 pF. Find the resistance. If the amplifier gain is 10, obtain the ratio of the resistances in the in the other arms. [5]
10. (a) Write a short note on Schmitt Trigger and also find the width of hysteresis loop. [5+3]
- (b) An inverting amplifier has a gain of 80 and it is used to amplify a sinusoidal input signal of variable frequency and maximum amplitude of 12.5 mV. Find the maximum operating frequency of the amplifier given that the slew rate is $2.5\text{ V}/\mu\text{s}$. [7]
11. (a) Explain with a circuit diagram the operation of a push-pull amplifier. Obtain an expression for the maximum efficiency of the amplifier. [9]
- (b) Describe with circuit diagram the action of i) emitter follower [3+3]
ii) Darlington pair.