



BRAINWARE UNIVERSITY

ODD Semester Examinations 2021- 22

Programme – Bachelor of Technology in Computer Science & Engineering - 2018 [B.Tech.(CSE)]

Course Name – Digital Electronics

Course Code – ESC(CSE)302

(Semester III)

Time allotted : 1 Hour 25 Minutes

Full Marks : 70

(Multiple choice type question)

70 x 1 = 70

Choose the correct alternative from the following

- (I) In an ECL the output is taken from _____.
- A) Emitter
B) Base
C) Collector
D) Junction of emitter and base
- (II) The odd parity output of decimal number 9 is
- A) 0
B) 1
C) 11
D) 1001
- (III) Let the input of a subtractor is A and B then what the output will be if A = B?
- A) 0
B) 1
C) A
D) B
- (IV) When an input signal A=11001 is applied to a NOT gate serially, its output signal is
- A) 111
B) 00110
C) 10101
D) 11001
- (V) Ripple counters are also called _____.
- A) SSI counters
B) Asynchronous counters
C) Synchronous counters
D) VLSI counters
- (VI) There are many situations in logic design in which simplification of logic expression is possible in terms of XOR and _____ operations.
- A) X-NOR
B) X-OR
C) NOR
D) NAND
- (VII) Which is an incorrect rule of binary subtraction from the following?
- A) $0 - 0 = 0$
B) $0 - 1 = -1$
C) $1 - 0 = 1$
D) $0 - 1 = 1$ with borrow '1'
- (VIII) A digital multiplexer is a combinational circuit that selects
- A) One digital information from several sources and transmits the selected one
B) Many digital information and convert them into one
C) Many decimal inputs and transmits the selected information
D) Many decimal outputs and accepts the selected information
- (IX) $(A + B)(A' * B') = ?$
- A) 1
B) 0
C) AB
D) AB'
- (X) In 1:4 demultiplexer, if $S_0 = 1$ & $S_1 = 1$, then the output will be _____.
- A) Y_0
B) Y_1
C) Y_2
D) Y_3
- (XI) The excess-3 code for 597 is given by _____.
- A) 100011001010
B) 100010100111

C) 10110010111

D) 10110101101

(XII) The first step of analysis procedure of SR latch is to _____

A) label inputs

B) label outputs

C) label states

D) label tables

(XIII) Which of the following circuits come under the class of sequential logic circuits? 1. Full adder 2. Full subtractor 3. Half adder 4. J-K flip 5. Counter

A) 1 and 2

B) 2 and 3

C) 3 and 4

D) 4 and 5

(XIV) $(734)_8 = (?)_{16}$

A) C1D

B) DC1

C) 1CD

D) 1DC

(XV) How many NOT gates are required for the construction of a 4-to-1 multiplexer?

A) 3

B) 4

C) 2

D) 5

(XVI) To increase fan-out of the gate in DTL

A) An additional capacitor may be used

B) An additional transistor and diode may be used

C) An additional resistor may be used

D) Only an additional diode may be used

(XVII) In a comparator, if we get input as $A > B$ then the output will be _____.

A) 1

B) 0

C) A

D) B

(XVIII) In which of the following base systems is 123 not a valid number?

A) Base16

B) Base3

C) Base10

D) Base8

(XIX) The largest two digit hexadecimal number is _____.

A) $(FE)_{16}$ B) $(FD)_{16}$ C) $(FF)_{16}$ D) $(EF)_{16}$

(XX) The output of a subtractor is given by (if A, B and X are the inputs) _____

A) $A \text{ AND } B \text{ XOR } X$ B) $A \text{ XOR } B \text{ XOR } X$ C) $A \text{ OR } B \text{ NOR } X$ D) $A \text{ NOR } B \text{ XOR } X$

(XXI) In RTL NOR gate, the output is at logic 1 only when all the inputs are at

A) logic 0

B) logic 1

C) +10V

D) Floating

(XXII) TTL circuits with "totem-pole" output stage minimize

A) The power dissipation in RTL

B) The time consumption in RTL

C) The speed of transferring rate in RTL

D) Propagation delay in RTL

(XXIII) A digital system consists of _____ types of circuits.

A) 2

B) 3

C) 4

D) 5

(XXIV) Which of the following is the Universal Flip-flop?

A) S-R flip-flop

B) J-K flip-flop

C) Master slave flip-flop

D) D Flip-flop

(XXV) Exclusive-OR (XOR) logic gates can be constructed from what other logic gates?

A) OR gates only

B) AND gates and NOT gates

C) AND gates, OR gates, and NOT gates

D) OR gates and NOT gates

(XXVI) In a multiplexer the output depends on its _____.

A) Data inputs

B) Select inputs

C) Select outputs

D) None of these

(XXVII) Divide the binary numbers: $111101 \div 1001$ and find the remainder

- A) 10
C) 1100
- B) 1010
D) 0011

(XXVIII) What is one disadvantage of an S-R flip-flop?

- A) It has no Enable input
C) It has no clock input
- B) It has a RACE condition
D) Invalid State

(XXIX) The selector inputs to an arithmetic/logic unit (ALU) determine the

- A) Selection of the IC
C) Data word selection
- B) Arithmetic or logic function
D) Clock frequency to be used

(XXX) How many stages a DTL consist of?

- A) 2
C) 4
- B) 3
D) 5

(XXXI) What does minuend and subtrahend denotes in a subtractor?

- A) Their corresponding bits of input
C) Its inputs
- B) Its outputs
D) Borrow bits

(XXXII) How many AND gates are required for a 8-to-1 multiplexer?

- A) 5
C) 8
- B) 7
D) 6

(XXXIII) Which logic is the fastest of all the logic families?

- A) TTL
C) HTL
- B) ECL
D) DTL

(XXXIV) In which operation, carry is obtained?

- A) Subtraction
C) Multiplication
- B) Addition
D) Addition and Subtraction

(XXXV) One multiplexer can take the place of _____

- A) Several SSI logic gates
C) Several Ex-NOR gates
- B) Combinational logic circuits
D) Several SSI logic gates or combinational logic circuits

(XXXVI) ECL's major disadvantage is that

- A) It requires more power
C) It creates more noise
- B) It's fan-out capability is high
D) It is slow

(XXXVII) The expression $Y=(A+B)(B+C)(C+A)$ shows the _____ operation.

- A) AND
C) SOP
- B) POS
D) NAND

(XXXVIII) A combinational circuit is one in which the output depends on the

- A) Input combination at the time
C) Input combination at that time and the previous input combination
- B) Input combination and the previous output
D) Present output and the previous output

(XXXIX) The logic circuits whose outputs at any instant of time depends only on the present input but also on the past outputs are called _____.

- A) Combinational circuits
C) Latches
- B) Sequential circuits
D) Flip-flops

(XL) The role of the _____ is to convert the collector current into a voltage in RTL.

- A) Collector resistor
C) Capacitor
- B) Base resistor
D) Inductor

(XLI) If the number of n selected input lines is equal to 2^m then it requires _____ select lines.

- A) 2
C) n
- B) m
D) 2n

(XLII) TTL is called transistor-transistor logic because both the logic gating function and the amplifying function are performed by _____.

- A) Resistors
C) One transistor
- B) Bipolar junction transistors
D) Resistors and transistors respectively
- (XLIII) The full form of TCTL is _____.
- A) Transistor-coupled transistor logic
C) Transistor-complemented transistor logic
- B) Transistor-capacitor transistor logic
D) Transistor-complementary transistor logic
- (XLIV) If minuend = 0, subtrahend = 1 and borrow input = 0 in a full subtractor then the difference output will be _____
- A) 1
C) Floating
- B) 0
D) High Impedance
- (XLV) In the toggle mode a JK flip-flop has-
- A) J = 0, K = 0
C) J = 0, K = 1
- B) J = 1, K = 1
D) J = 1, K = 0
- (XLVI) In a combinational circuit, the output at any time depends only on the _____ at that time.
- A) Voltage
C) Input values
- B) Intermediate values
D) Clock pulses
- (XLVII) The full subtractor can be implemented using _____.
- A) Two XOR and an OR gates
C) Two multiplexers and an AND gate
- B) Two half subtractors and an OR gate
D) Two comparators and an AND gate
- (XLVIII) Karnaugh map is used:
- A) To draw the digital circuit layout
C) To locate different gates in a digital circuit
- B) To simplify logical function
D) None of these
- (XLIX) Standard TTL circuits operate with a __ volt power supply
- A) 2
C) 4
- B) 5
D) 6
- (L) Which of the following describes the operation of a positive edge-triggered D flip-flop?
- A) If both inputs are HIGH, the output will toggle
C) When both inputs are LOW, an invalid state exists
- B) The output will follow the input on the leading edge of the clock
D) The input is toggled into the flip-flop on the leading edge of the clock and is passed to the output on the trailing edge of the clock
- (LI) All logic operations can be obtained by means of _____.
- A) AND and NAND operations
C) OR and NOT operations
- B) OR and NOR operations
D) NAND and NOR operations
- (LII) Which of the following flip-flop is used as a latch?
- A) J-K flip-flop
C) T flip-flop
- B) R-S flip-flop
D) D flip-flop
- (LIII) Don't care conditions can be used for simplifying Boolean expressions in _____.
- A) Registers
C) K-maps
- B) Terms
D) Latches
- (LIV) A 4-bit shift register that receives 4 bits of parallel data will shift to the _____ by _____ position for each clock pulse.
- A) Right, one
C) Left, one
- B) Right, two
D) Left, three
- (LV) The NOR gate output will be high if the two inputs are _____.
- A) 0 0
C) 1 0
- B) 0 1
D) 1 1
- (LVI) If A, B and C are the inputs of a full adder then the carry is given by _____
- A) A AND B OR (A OR B) AND C
C) (A AND B) OR (A AND B)C
- B) A OR B OR (A AND B) C
D) A XOR B XOR (A XOR B) AND C
- (LVII) Binary subtraction of 100101 – 011110 is
- A) 000111
C) 111000
- B) 10101
D) 101010

- (LVIII) On subtracting $(001100)_2$ from $(101001)_2$ using 2's complement, we get _____.
- A) 1101100
B) 011101
C) 11010101
D) 11010111
- (LIX) The digit 10001 in Binary system is equivalent to in Hexadecimal system
- A) 10
B) 11
C) D
D) F
- (LX) For arithmetic operations which one is faster?
- A) 1's complement
B) 2's complement
C) 10's complement
D) 9's complement
- (LXI) The canonical sum of product form of the function $y(A,B) = A + B$ is
- A) $AB + BB + A'A$
B) $AB + AB' + A'B$
C) $BA + BA' + A'B'$
D) $AB' + A'B + A'B'$
- (LXII) When two 16-input multiplexers drive a 2-input MUX, what is the result?
- A) 2-input MUX
B) 4-input MUX
C) 16-input MUX
D) 32-input MUX
- (LXIII) If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be _____
- A) SET
B) RESET
C) Clear
D) Invalid
- (LXIV) The binary number 10101 is equivalent to decimal number _____.
- A) 19
B) 12
C) 21
D) 27
- (LXV) What is an ambiguous condition in a NAND based S'-R' latch?
- A) $S'=0, R'=1$
B) $S'=1, R'=0$
C) $S'=1, R'=1$
D) $S'=0, R'=0$
- (LXVI) The inverter can be produced with how many NAND gates?
- A) 1
B) 3
C) 2
D) 4
- (LXVII) The excess 3 code of decimal number 26 is _____.
- A) 0100 1001
B) 1011001
C) 1000 1001
D) 1001101
- (LXVIII) The gates required to build a half adder are _____.
- A) EX-OR gate and NOR gate
B) EX-OR gate and OR gate
C) EX-OR gate and AND gate
D) EX-NOR gate and AND gate
- (LXIX) The value of base x is: $(211)_x = (152)_8$
- A) 7
B) 8
C) 6
D) 5
- (LXX) To add two m-bit numbers, the required number of half adders is
- A) $2m - 1$
B) $m - 1$
C) $2m + 1$
D) $2m$