



BRAINWARE UNIVERSITY

Term End Examination 2018 - 19

Programme – B.Sc. (Honours) in Computer Science

Course Name – Analog Electronic Circuits

Course Code – BECE010602

(Semester – 1)

Time allotted: 3 Hours

Full Marks: 70

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group –A

(Multiple Choice Type Question)

10 x 1 = 10

1. *Choose the correct alternative from the following*

(i) At 0K an intrinsic semiconductor behaves like

- a. super conductor
- b. insulator
- c. semiconductor
- d. p-type semiconductor

(ii) A Si diode operating at room temperature has the reverse saturation current in the order of

- a. mA
- b. μA
- c. nA
- d. A

(iii) In BJT, $I_c = 10 \text{ mA}$ for $I_b = 100 \mu\text{A}$, the approximate value of β is

- a. 100
- b. 10
- c. 1000
- d. 1

(iv) Most heavily doped region in BJT is the

- a. emitter
- b. base
- c. collector
- d. none of these

- (v) If $\alpha = 0.98$, then β is equal to
- | | |
|---------|--------|
| a. 0.49 | b. 49 |
| c. 50 | d. 0.5 |
- (vi) Wein Bridge Oscillator is used in the range
- | | |
|------------------------------|------------------------|
| a. Audio frequency | b. Radio frequency |
| c. Very high frequency (VHF) | d. Microwave frequency |
- (vii) Which of the following devices is expected to have the highest input impedance
- | | |
|-----------|----------|
| a. MOSFET | b. FET |
| c. BJT | d. OPAMP |
- (viii) The transconductance of a FET is
- | | |
|---|--------------------------------------|
| a. directly proportional to $\sqrt{V_{DS}}$ | b. directly proportional to I_{DS} |
| c. directly proportional to $\sqrt{I_{DS}}$ | d. none of these |
- (ix) FET is a
- | | |
|--------------------------------|---------------------------------|
| a. voltage controlled device | b. current controlled device |
| c. impedance controlled device | d. resistance controlled device |
- (x) The common mode rejection ratio of an OP AMP is
- | | |
|----------------------------|---------------------------|
| a. much smaller than unity | b. much larger than unity |
| c. unity | d. none of these |

Group – B


(Short Answer Type Questions)

3 x 5 = 15

Answer any *three* from the following

2. With the help of the energy band diagram, differentiate between metal, insulator and semiconductor. 5
3. Find out the relation between α and β for a transistor, where notations have their usually meanings. Find α and I_C of a transistor with $\beta = 49$ and $I_E = 12$ mA. 3+2

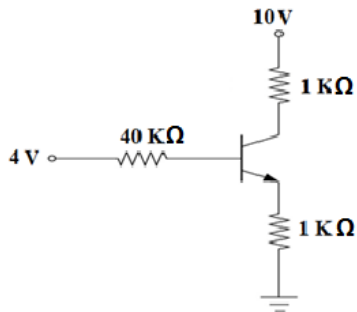4. Sketch the structure of a p channel depletion type MOSFET. Explain how the depletion region is produced in the channel. Can a depletion MOSFET work in the enhancement mode? If so how? 5
5. Calculate the output voltage for the summing amplifier circuit using OPAMP. Given $V_1=0.2V$, $V_2=2V$, $V_3=1V$ and $R_1=5K\Omega$, $R_2=20K\Omega$, $R_3=50K\Omega$ and $R_f=30K\Omega$, where notations carry the usual significance. 5
6. The CE configuration of an n-p-n transistor is shown in the figure where $V_{BE} = 0.7V$ and $V_{CE} = 0.2V$. If the emitter current is 3 mA, find out the collector current and the base current. 5



Group – C


(Long Answer Type Questions)

3 x 15 = 45

Answer any *three* from the following

7. (a) Derive an expression for conductivity of a semi-conductor in terms of carrier concentration. 5
- (b) At 300K the intrinsic concentration of silicon is $1.5 \times 10^{16} \text{ m}^{-3}$. If the electron and the hole mobilities are $0.13 \text{ m}^2/(\text{Vs})$ and $0.05 \text{ m}^2/(\text{Vs})$ respectively, determine the intrinsic conductivity and resistivity of silicon at 300K. 5
- (c) Draw the circuit diagram of a full wave rectifier using p-n junction diodes and explain its operation. 5

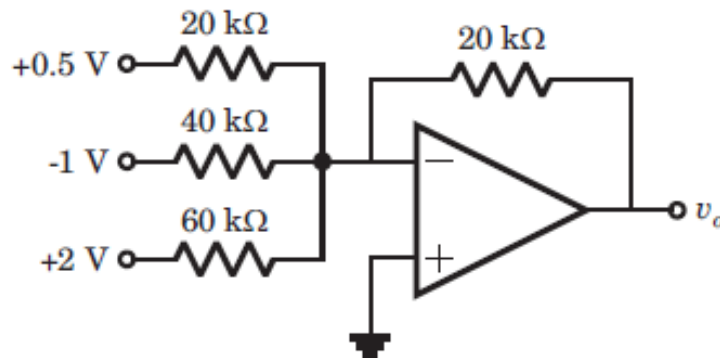8. (a) Illustrate the formation of depletion region in p-n junction diode. Write down Shockley's equation, stating the meanings of different terms used stand for. 3+2
- (b) The reverse saturation current at 300 K of a p-n junction Ge diode is $5 \mu\text{A}$. Find the voltage to be applied across the junction to obtain a forward current of 50 mA. (Mass of electron= 1.6×10^{-19} kg; Boltzmann Constant= 1.38×10^{-23} J/k) 5
- (c) A p-n junction Ge diode has reverse saturation current of $1.5 \mu\text{A}$ at 300 K. Obtain d.c and a.c. resistances of diode at forward bias of 0.3 V. 1+4
9. (a) Explain with the help of a block diagram, the working principle of a feedback amplifier. Hence deduce Barkhausen criterion of oscillation for both positive and negative feedback. 7+2
- (b) Illustrate the merits of negative feedback in amplifier. 2
- (c) An amplifier has voltage gain equal to -100. The feedback ratio is -0.04. Find i) Voltage gain with feedback, ii) the output voltage of feedback amplifier for an input voltage of 40 mV, iii) the feedback factor and iv) the feedback voltage. 4
10. (a) Explain different current components of a transistor. 5
- (b) A n-p-n transistor is operating in CE mode. Calculate V_{CE} if $\beta = 125$. Take $V_{BE} = 0.6\text{V}$, V_{BB} (base supply voltage)= 10 V, V_{CC} (collector supply voltage) = 20 V, R_B = (series resistance in base circuit) = 310 k Ω and R_C = (series resistance in collector circuit)= 5 k Ω . 5
- (c) For a transistor, $I_C = 7\text{mA}$, $I_{CO} = 25 \mu\text{A}$ and $I_B = 0.1\text{mA}$, calculate α , β and I_E , where notations carry their usual meanings. 5
11. (a) Describe the use of an OPAMP as differentiator. 5
- (b) Find out the output voltage v_o and voltage gain of the circuit given below 5



- (c) A 5 mV, 1 KHz sinusoidal signal is applied to the input of an OPAMP integrator for which $R = 100 \text{K}\Omega$ and $C = 1 \mu\text{F}$. Calculate output voltage. 5