



BRAINWARE UNIVERSITY

Term End Examination 2024-2025

Programme – BCA-Hons-2024

Course Name – Digital Logic

Course Code - BCA17101 (T)

(Semester I)

Library
Brainware University
398, Ramkrishnapur Road, Barasat
Kolkata, West Bengal-700125

Full Marks : 40

Time : 2:0 Hours

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

(Multiple Choice Type Question)


1 x 10=10

1. Choose the correct alternative from the following :

- (i) Which of the following is the signed 8-bit binary representation for the decimal value -20?
 - a) 10100
 - b) 11101110
 - c) 11101111
 - d) 11101100
- (ii) When the output of two input AND gate is high?
 - a) all inputs are high
 - b) all inputs are low
 - c) at least one input is high
 - d) None of these
- (iii) Identify for which of the following binary code two subsequent values only differ in one bit.
 - a) BCD
 - b) Excess-3 code
 - c) Gray Code
 - d) None of these
- (iv) Identify the proper form of a logical expression $Y = (A+B)(B+C')(A'+C)$.
 - a) SOP
 - b) POS
 - c) Both of these
 - d) None of these
- (v) What is the equivalent binary number of the octal number (753) ?
 - a) 1011000001
 - b) 101101100
 - c) 111101011
 - d) 10101100011
- (vi) In an SR flip-flop, if both S and R inputs are 0, what will be the output state?
 - a) Set
 - b) Reset
 - c) No Change
 - d) Invalid State
- (vii) What is the primary function of the clock input in a flip-flop?
 - a) It sets the output to high.
 - b) It synchronizes the flip-flop's state changes.
 - c) It toggles the output state.
 - d) It resets the flip-flop to its initial state.
- (viii) On subtracting 001100 from 101001 using 2's complement, select we get
_____.

- a) 11101
c) 11100
(ix) Choose the expression $(A \oplus B)'$ is equal to:
a) $A \oplus B$.
c) $A' \oplus B$.
(x)

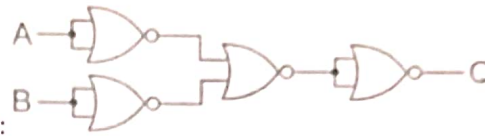- b) 1101100
d) 11011
b) $A + B$.
d) $A' + B$.



Choose the output of the given logic circuit:

- a) OR
c) AND
b) NOR
d) NAND

Group-B

(Short Answer Type Questions)

3 x 5=15

2. Describe the main difference between a combinational circuit and a sequential circuit. (3)
3. What is an SR flip-flop? (3)
4. Write a short note on De-Morgan's Law. (3)
5. Generalize the following expressions using K-map: (i) $F = \sum m(0,1,3,5,6,11,15)$. (ii) $F = \sum m(0,1,2,5,6)$. (3)
6. Assess consensus theorem in Boolean algebra. (3)

OR

Determine the concept of hazard in digital circuits. (3)

Group-C

(Long Answer Type Questions)

5 x 3=15

7. Enumerate the Boolean expression using K-MAP $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$. (5)
8. Show the truth table and logic diagram of a Full Adder. How does it differ from a Half Adder? (5)
9. Evaluate the significance of select lines in a Multiplexer and how they determine the output. (5)

OR

Explain the operation of a 1-to-8 Demultiplexer. Conclude with its truth table and logic diagram. (5)
