



Library
Brainware University
398, Ramkrishnapur Road, Barasat
Kolkata, West Bengal-700125

BRAINWARE UNIVERSITY

Term End Examination 2024-2025
Programme – BCA(MAWT)-Hons-2024
Course Name – Digital Logic
Course Code - BMT17201 (T)
(Semester I)

Full Marks : 40

Time : 2:0 Hours

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

(Multiple Choice Type Question)

1 x 10=10

1. Choose the correct alternative from the following :

- (i) Show the octal number representation of Decimal 0.345.
 - a) 0.2404
 - b) 0.2605
 - c) 0.1945
 - d) 0.1605
- (ii) Find binary equivalent of the octal number 725.
 - a) 111101101
 - b) 111011101
 - c) 111101010
 - d) 111010101
- (iii) Which digital code is a reflective code used primarily in analog-to-digital converters?
 - a) BCD
 - b) Excess-3 Code
 - c) Gray Code
 - d) ASCII
- (iv) What is the range of values that can be represented by an 8-bit unsigned binary number?
 - a) -256 to 255
 - b) 0 to 127
 - c) -128 to 127
 - d) 0 to 255
- (v) Select output of a full subtractor is same as-
 - a) Decoder
 - b) Half subtractor
 - c) Full adder
 - d) Half adder
- (vi) Select how the sum output is calculated in a half-adder when the inputs are A and B.
 - a) A EXNOR B
 - b) A EXOR B
 - c) A OR B
 - d) A AND B
- (vii) Which of the following logic gates can be used to implement a 2-to-1 multiplexer?
 - a) NAND gates
 - b) NOR gates
 - c) AND, OR, and NOT gates
 - d) XOR gates
- (viii) How many inputs are required for a 4-to-16 decoder?
 - a) 5
 - b) 4
 - c) 3
 - d) 2

(ix) Identify the related expression for Absorption law in Boolean expression.

- a) $A+AB=A$
c) $A+AB=BA$

- b) $AB+AA'=A$
d) $A+B=B+A$

(x) Apply Boolean Law, then $A+1 = \underline{\hspace{1cm}}$.

- a) 1
c) 0

- b) A
d) A'

Group-B

(Short Answer Type Questions)

3 x 5=15

2. Explain flip-flops.

(3)

3. What is a logic gate? List the basic types of logic gates.

(3)

4. Simplify the following Boolean expression: $(A+B).(A+B')$.

(3)

5. a) Convert 59.7210 to BCD. b) Convert 8B3F16 to binary.

(3)

6. Examine how De Morgan's Theorem simplify Boolean expressions.

(3)

OR

Infer the significance of the Karnaugh map (K-map) in Boolean algebra.

(3)

Group-C

(Long Answer Type Questions)

5 x 3=15

7. Find the truth table of the function : (a) $F = xy + xy' + y'z$ and (b) $F = x'z' + yz$.

(5)

8. Develop the simplified form of the boolean function $F(A,B,C,D) = \sum(1,5,9,10,11,14,15)$ using four-variable maps.

(5)

9. Evaluate the significance of select lines in a Multiplexer and how they determine the output.

(5)

OR

Explain the operation of a 1-to-8 Demultiplexer. Conclude with its truth table and logic diagram.

(5)

Library
Brainware University
398, Ramkrishnapur Road, Barasat
Kolkata, West Bengal-700125