



- a) Zero
c) Positive
- b) Negative
d) Equal to V_P
- (viii) Select, The voltage gain of an ideal voltage follower is
a) 1
c) 0
- b) <1
d) infinity
- (ix) The voltage follower is commonly used as
a) Switch
c) Regulator
- b) Isolator
d) None of these
- (x) A JFET has the following parameters: $I_{DSS} = 32 \text{ mA}$; $V_{GS}(\text{off}) = -8 \text{ V}$; $V_{GS} = -4.5 \text{ V}$. Find the value of drain current.
- a) 6 mA
c) 6.21 mA
- b) 6.12 mA
d) None of these
- (xi) Identify, Inverting op-amp is
a) Voltage shunt feedback
c) Current series feedback.
- b) Voltage series feedback
d) Current shunt feedback
- (xii) Choose the correct option: Instrumentation amplifiers are used primarily in
a) High noise environment
c) Test instruments
- b) Medical equipment
d) Filter circuits.
- (xiii) When a JFET operates above pinch-off voltage,
a) Drain current remains constant
c) Drain current decreases gradually
- b) Drain current increases rapidly
d) Depletion region becomes zero
- (xiv) Which of the following are the non-linear applications of OP-AMP?
a) Current-to-voltage converter
c) Peak detector
- b) Comparator
d) Limiter
- (xv) If FET operates in cut-off, the depletion layers are
a) Touching each other
c) Far apart
- b) Close together
d) None of these

Group-B

(Short Answer Type Questions)

3 x 5=15

2. Discuss, why does CE configuration provide large current amplification. (3)
3. Explain the design of first order high pass filter. (3)
4. Write, why BJT is called current controlled device? (3)
5. Establish the major difference between a bipolar & unipolar device? (3)
6. Compare RC oscillators with LC oscillators. (3)

OR

- Explain barkhausen criteria as applicable to oscillator circuits. (3)

7. Write the characteristics of CE configuration. (5)
8. Explain the input and output characteristics of a transistor in CB configuration. (5)
9. Express the relationship between α , β and γ of a transistor. (5)
10. State the advantage and disadvantage of negative feedback amplifier. (5)
11. Explain the operation of op-amp comparator with waveforms. (5)
12. Draw & explain RC phase shift oscillator. (5)

OR

Explain the working of collpitts oscillator. (5)
