



17592

**BRAINWARE UNIVERSITY**

Library
Brainware University
398, Ramkrishnapur Road, Barasat
Kolkata, West Bengal-700125

Term End Examination 2024-2025**Programme – B.Tech.(CSE)-DS-2024/B.Tech.(CSE)-CYS-2024****Course Name – Applied Digital Logic Design****Course Code - BES00018****(Semester II)****Full Marks : 60****Time : 2:30 Hours**

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A**(Multiple Choice Type Question)****1 x 15=15****1. Choose the correct alternative from the following :****(i) Select the binary equivalent of the decimal number 368**

a) 101110000

b) 110110000

c) 111010000

d) 111100000

(ii) Select hexadecimal equivalent number of octal number 734

a) C 1 D

b) D C 1

c) 1 C D

d) 1 D C

(iii) Select the decimal equivalent of hex number 1A53

a) 6793

b) 6739

c) 6973

d) 6379

(iv) Identify which one of the following is a major difference between a half adder and a full adder

a) Full-adders are made up of two half-adders

b) Full adders can handle double-digit numbers

c) Full adders have a carry input capability

d) Half adders can handle only single-digit numbers

(v) Estimate how many basic binary subtraction operations are possible?

a) 1

b) 4

c) 3

d) 2

(vi) Relate the statement "When performing subtraction by addition in the 2's-complement system _____"

a) The minuend and the subtrahend are both changed to the 2's-complement

b) The minuend is changed to 2's-complement and the subtrahend is left in its original form

- c) The minuend is left in its original form and the subtrahend is changed to its 2's-complement
- d) The minuend and subtrahend are both left in their original form
- (vii) Choose the correct option which is a type of digital logic circuit
- a) Combinational logic circuits
- b) Sequential logic circuits
- c) Both a & b
- d) None of the mentioned
- (viii) Choose digital logic circuits can be used to add more than 1 – bit simultaneously
- a) Full – adder
- b) Ripple – carry adder
- c) Half – adder
- d) Serial adder
- (ix) Choose the following is true for a full-subtractor circuit
- a) It has two inputs and one output.
- b) It performs subtraction considering borrow from the previous stage.
- c) It performs subtraction without borrow.
- d) It is used only for multi-bit subtraction.
- (x) Choose the main function of a latch
- a) Store multiple bits of data
- b) Perform arithmetic operations
- c) Temporarily store a single bit of data
- d) Act as a power amplifier
- (xi) Choose the output from a D flip-flop if D = 1 and the clock is low
- a) No change
- b) Toggle between 0 and 1
- c) 0
- d) 1
- (xii) Choose the gate which is placed between clock input and the input of AND gate to convert a positive level triggered flip – flop to a negative level triggered flip – flop
- a) NOR gate
- b) NOT gate
- c) Buffer
- d) NAND gate
- (xiii) Identify the output of an even parity checker if the total number of 1s in the input data is odd
- a) High (1)
- b) Low (0)
- c) Undefined
- d) Depends on the circuit design
- (xiv) Identify the output of a demultiplexer when the select lines are set to a specific binary value.
- a) All outputs are activated.
- b) Only the corresponding output line is activated.
- c) The output is always high.
- d) The output depends on the enable signal only.
- (xv) Identify the IC can be used as a 3-to-8 decoder
- a) 74138
- b) 74151
- c) 74154
- d) 7404

Group-B

(Short Answer Type Questions)

3 x 5=15

2. Apply Boolean algebra to simplify the expression

(3)

$$Y = \overline{A} \cdot B + A \cdot \overline{B} + \overline{A} \cdot \overline{B}$$

3. Illustrate the difference between asynchronous and synchronous counter

(3)

4. Convert the Octal number 237677 to a Hexadecimal Number (3)
 5. Construct 1 line to 4 line demultiplexer. (3)
 6. Compare volatile and Non-Volatile memory. (3)

Library
 Brainware University
 Ramkrishnapur Road, Barasat
 Pin-700125

OR

Explain SISO register. (3)

Group-C

(Long Answer Type Questions)

5 x 6=30

7. Identify the simplified boolean expression of the following function using K-Map (5)

$$F = \sum m(2, 3, 4, 5, 6, 7, 9, 12, 13, 14, 15)$$

8. Represent the following Boolean expression using basic gates (5)

$$Y = AB + BC + AC$$

9. Describe decimal number 3.248×10^4 to a single-precision floating-point binary number. (5)

10. Explain the conversion technique of JK flip-flop to D flip-flop. (5)

11. Explain the fundamental principles of Read-Only Memory (ROM), and illustrate how data is stored and retrieved from ROM cells. Write about a specific application where ROM is commonly used. (5)

12. Construct 4:1 Multiplexer using 2:1 Multiplexer and one OR gate (5)

OR

Construct 8:1 multiplexer using 4:1 multiplexer and OR gate. (5)
