



17015



LIBRARY
Brainware University
Barasat, Kolkata -700125

BRAINWARE UNIVERSITY

Term End Examination 2024-2025

Programme – Dip.RA-2022

Course Name – Industrial Electronics

Course Code - ECPC601

(Semester VI)

Full Marks : 60

Time : 2:30 Hours

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

(Multiple Choice Type Question)

1 x 15=15

1. Choose the correct alternative from the following :

- (i) Choose the reason why switching regulators are preferred over linear regulators in power-sensitive applications
 - a) Higher power dissipation
 - b) Lower efficiency
 - c) High efficiency and low heat
 - d) Expensive and large size
- (ii) Select the role of a diode in a buck converter circuit.
 - a) Blocks input voltage
 - b) Acts as a freewheeling diode
 - c) Provides isolation
 - d) Reduces switching losses
- (iii) Indicate the major drawback of a boost converter.
 - a) Low efficiency
 - b) Requires complex control
 - c) No voltage step-up
 - d) High voltage ripple
- (iv) Identify the key difference between a buck and a boost converter.
 - a) Buck steps down voltage, boost steps up
 - b) Both step up voltage
 - c) Both step down voltage
 - d) None
- (v) Select the main reason for using a buck-boost converter.
 - a) Only steps up voltage
 - b) Can step up or down voltage
 - c) Provides positive output only
 - d) None
- (vi) Define the diode is operating at a high frequency. Which parameter is most critical?
 - a) Reverse recovery time
 - b) Forward voltage drop
 - c) Thermal resistance
 - d) Breakdown voltage
- (vii) Define the thermal resistance of a diode can be reduced by.
 - a) Increasing ambient temperature
 - b) Using a heat sink
 - c) Reducing forward voltage drop
 - d) Increasing the reverse voltage rating
- (viii) Discuss the power diodes are generally made of.
 - a) Silicon
 - b) Germanium
 - c) Gallium arsenide
 - d) Copper
- (ix) Discuss the forward voltage drop of a silicon power diode is approximately.

- Page 2 of 2