



## BRAINWARE UNIVERSITY

### Term End Examination 2020 - 21

Programme – Bachelor of Technology in Electronics & Communication Engineering

Course Name – Network Theory

Course Code - PCC-EC304

Semester / Year - Semester III

Time allotted : 75 Minutes

Full Marks : 60

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

### Group-A

(Multiple Choice Type Question)

1 x 60=60

1. (Answer any Sixty )

(i) Unit of inductance is \_\_\_\_\_

- |          |          |
|----------|----------|
| a) Weber | b) Henry |
| c) Farad | d) Tesla |

(ii) The current law represents a mathematical statement of fact that

- |                                      |                                     |
|--------------------------------------|-------------------------------------|
| a) voltage cannot accumulate at node | b) charge cannot accumulate at node |
| c) charge at the node is infinite    | d) none of these                    |

(iii) The circuit in which current has a complete path to flow is called \_\_\_\_\_ circuit.

- |           |              |
|-----------|--------------|
| a) Short  | b) Open      |
| c) closed | d) open loop |

(iv) Potential difference in electrical terminology is known as?

- |               |                |
|---------------|----------------|
| a) Voltage    | b) Current     |
| c) Resistance | d) Conductance |

(v) If the voltage-current characteristics are a straight line through the origin, then the element is said to be?

- |                   |                       |
|-------------------|-----------------------|
| a) Linear element | b) Non-linear element |
|-------------------|-----------------------|

c) Unilateral element

d) Bilateral element

(vi) For a voltage source to be neglected, the terminals across the source should be

a) replaced by inductor

b) short circuited

c) replaced by some resistance

d) open circuited

(vii) A dependent source

a) is always a voltage source

b) may be a current source or a voltage source

c) is always a current source

d) none of the mentioned

(viii) Consider a circuit with two unequal resistances in parallel, then

a) large current flows in large resistor

b) current is same in both

c) potential difference across each is same

d) smaller resistance has smaller conductance

(ix) In which of the following cases is Ohm's law not applicable?

a) Electrolytes

b) Arc lamps

c) Insulators

d) Vacuum ratio values

(x) In Superposition theorem, while considering a source, all other voltage sources are?

a) open circuited

b) short circuited

c) change its position

d) removed from the circuit

(xi) In Superposition theorem, while considering a source, all other current sources are?

a) open circuited

b) short circuited

c) change its position

d) removed from the circuit

(xii) To check for the Reciprocity Theorem we consider \_\_\_\_\_ of response to excitation.

- a) Ratio
- b) Addition
- c) product
- d) Subtraction

(xiii) The circuit which satisfies Reciprocity Theorem is called?

- a) Short circuit
- b) Open circuit
- c) Linear circuit
- d) Non-linear circuit

(xiv) If  $Z_L = Z_S^*$ , then?

- a)  $R_L = 1$
- b)  $R_L = 0$
- c)  $R_L = -R_S$
- d)  $R_L = R_S$

(xv) For  $Z_L = Z_S^*$ , the relation between  $X_L$  and  $X_S$  is?

- a)  $X_L = X_S$
- b)  $X_L = 0$
- c)  $X_L = 1$
- d)  $X_L = -X_S$

(xvi) The efficiency in case of maximum power transfer theorem is

- a) 100 %.
- b) less than 50 %.
- c) 50 %.
- d) 50 % - 100 %.

(xvii) If there are  $N$  nodes in a circuit, then the number of nodal equations that can be formed are?

- a)  $N+1$
- b)  $N$
- c)  $N-1$
- d)  $N-2$

(xviii) If  $Z_S = R_S + jX_S$ ,  $Z_L = R_L + jX_L$ , then if  $R_L$  is fixed, the condition for maximum power to be transferred is?

- a)  $X_S = X_L$
- b)  $X_S + X_L = 0$
- c)  $X_S = -X_L$
- d) None of these

(xix) In a series resonance circuit, series resonance occurs when?

- a)  $X_L = 1$
- b)  $X_L = X_C$
- c)  $X_C = 1$
- d)  $X_L = -X_C$

(xx) As  $X_L = X_C$  in a series resonance circuit, the impedance is \_\_\_\_\_

- a) purely capacitive
- b) purely resistive
- c) purely inductive
- d) capacitive and inductive

(xxi) What is the disadvantage of exponential Fourier series?

- a) It is not easily visualized
- b) It cannot be easily visualized as sinusoids
- c) It is tough to calculate
- d) It is hard for manipulation

(xxii) Fourier series uses which domain representation of signals?

- a) Time domain representation
- b) Frequency domain representation
- c) Both combined
- d) Neither depends on the situation

(xxiii) How does Fourier series make it easier to represent periodic signals?

- a) Harmonically related
- b) Sinusoidally related
- c) Periodically related
- d) Exponentially related

(xxiv) How do we represent a pairing of a periodic signal with its fourier series coefficients in case of continuous time fourier series?

- a)  $x(t) ? X_n$
- b)  $x(t) ? X_{n+1}$
- c)  $x(t) ? X$
- d)  $x(n) ? X_n$

(xxv) What are the properties of continuous time fourier series?

- a) Linearity, time shifting
- b) Linearity, time shifting, frequency shifting
- c) Linearity, time shifting, frequency shifting, time reversal, time scaling,
- d) Linearity, time shifting, frequency shifting, time reversal, time scaling,

periodic convolution

periodic convolution, multiplication,  
differentiation

(xxvi) If  $x(t)$  and  $y(t)$  are two periodic signals with coefficients  $X_n$  and  $Y_n$  then the linearity is represented as?

a)  $ax(t) + by(t) = aX_n + bY_n$

b)  $ax(t) + by(t) = X_n + bY_n$

c)  $ax(t) + by(t) = aX_n + Y_n$

d)  $ax(t) + by(t) = X_n + Y_n$

(xxvii) What is the frequency shifting property of continuous time fourier series?

a) Multiplication in the time domain by a real sinusoid

b) Multiplication in the time domain by a complex sinusoid

c) Multiplication in the time domain by a sinusoid

d) Addition in the time domain by a complex sinusoid

(xxviii) In delta-connected system, the currents  $I_R$ ,  $I_Y$ ,  $I_B$  are equal in magnitude and they are displaced by \_\_\_\_\_ from one another.

a)  $90^\circ$

b)  $120^\circ$

c)  $60^\circ$

d)  $0^\circ$

(xxix) In a delta connected system, the expression of power (P) is?

a)  $V_L I_L \cos \phi$  W

b)  $3\sqrt{3} V_L I_L \cos \phi$  W

c)  $\sqrt{3} V_L I_L \cos \phi$  W

d)  $3 V_L I_L \cos \phi$  W

(xxx) Form factor for a sine wave is

a) 1.414

b) 0.707

c) 0.637

d) 1.11

(xxxi) If the resistors of star connected system are  $Z_R$ ,  $Z_Y$ ,  $Z_B$  then the impedance  $Z_{BR}$  in delta connected system will be?

a)  $(Z_R Z_Y + Z_Y Z_B + Z_B Z_R) / Z_B$

b)  $(Z_R Z_Y + Z_Y Z_B + Z_B Z_R) / (Z_B + Z_R)$

c)  $(Z_R Z_Y + Z_Y Z_B + Z_B Z_R) / Z_R$

d)  $(Z_R Z_Y + Z_Y Z_B + Z_B Z_R) / Z_Y$

(xxxii) In star connected system,  $V_{RY}$  is equal to?

- a)  $V_{YR}$
- b)  $-V_{YR}$
- c)  $2V_{YR}$
- d)  $3V_{YR}$

(xxxiii) The relation between  $V_{RY}$ ,  $V_{ph}$  in a star connected system is?

- a)  $V_{RY} = V_{ph}$
- b)  $V_{RY} = \sqrt{3}V_{ph}$
- c)  $V_{RY} = 3\sqrt{3}V_{ph}$
- d)  $V_{RY} = 3V_{ph}$

(xxxiv) Laplace transform changes the \_\_\_\_\_ domain function to the \_\_\_\_\_ domain function.

- a) time, time
- b) time, frequency
- c) frequency, time
- d) frequency, frequency

(xxxv) In the bilateral Laplace transform, the lower limit is?

- a) 0
- b) 1
- c) ?
- d) - ?

(xxxvi) The voltage and current in a capacitor are related as?

- a)  $i = C \frac{dv}{dt}$
- b)  $v = C \frac{dv}{dt}$
- c)  $i = C \frac{dv}{dt}$
- d)  $v = C \frac{dv}{dt}$

(xxxvii) The s-domain equivalent of the capacitor reduces to a capacitor with impedance?

- a)  $sC$
- b)  $C$
- c)  $1/C$
- d)  $1/sC$

(xxxviii) From the circuit shown below, find the value of current in the loop

- a)  $(V/R)/(s+1/RC)$
- b)  $(V/C)/(s+1/R)$
- c)  $(V/C)/(s+1/RC)$
- d)  $(V/R)/(s+1/R)$

(xxxix) After taking the inverse transform of current in the circuit shown

below, the value of current is?

- a)  $i=(V/C)e^{-t/R}$
- b)  $i=(V/C)e^{-t/RC}$
- c)  $i=(V/R)e^{-t/RC}$
- d)  $i=(V/R)e^{-t/R}$

(xl) The voltage across the resistor in the circuit shown below is?

- a)  $Ve^{t/R}$
- b)  $Ve^{-t/RC}$
- c)  $Ve^{-t/R}$
- d)  $Ve^{t/RC}$

(xli) The transfer function of a system having the input as  $X(s)$  and output as  $Y(s)$  is?

- a)  $Y(s)/X(s)$
- b)  $Y(s) * X(s)$
- c)  $Y(s) + X(s)$
- d)  $Y(s) - X(s)$

(xlii) The real part of the complex frequency is called?

- a) radian frequency
- b) neper frequency
- c) sampling frequency
- d) angular frequency

(xliii) The imaginary part of the complex frequency is called?

- a) angular frequency
- b) sampling frequency
- c) neper frequency
- d) radian frequency

(xliv) The transform impedance of the inductor is?

- a)  $L$
- b)  $1/L$
- c)  $sL$
- d)  $1/sL$

(xlv) The transform admittance of the inductor is?

- a)  $1/sL$
- b)  $sL$
- c)  $1/L$
- d)  $L$

(xlvi) The value of  $Z_1Z_2$  in the circuit shown below is?

- a)  $L/C$
- b)  $C/L$

c)  $1/LC$

d)  $LC$

(xlvii) The cut-off frequency of the low pass filter is?

a)  $1/\sqrt{LC}$

b)  $1/(\sqrt{LC})$

c)  $\sqrt{LC}$

d)  $\sqrt{LC}$

(xlviii) The scale factor is denoted by the letter?

a) G

b) H

c) I

d) J

(xlix) The zeros in the transfer function are denoted by?

a) 3

b) 2

c) 1

d) 0

(l) The network function  $N(S)$  becomes \_\_\_\_\_ when  $s$  is equal to anyone of the zeros.

a) 1

b) 2

c) 0

d) ?

(li) The  $N(S)$  becomes \_\_\_\_\_ when  $s$  is equal to any of the poles.

a) ?

b) 0

c) 1

d) 2

(lii) The coefficients in the numerator polynomial of the transfer function may be?

a) must be negative

b) must be positive

c) may be positive

d) may be negative

(liii) The degree of numerator polynomial in a transfer function may be as small as \_\_\_\_\_ independent of the degree of the denominator polynomial.

a) 1

b) 2



c) 0

d) 3

(liv) Two ports containing no sources in their branches are called?

a) active ports

b) passive ports

c) one port

d) three port

(lv) Two ports containing sources in their branches are called?

a) three port

b) one port

c) passive ports

d) active ports

(lvi) The value of one decibel is equal to?

a) 0.115 N

b) 0.125 N

c) 0.135 N

d) 0.145 N

(lvii) A filter which passes without attenuation all frequencies up to the cut-off frequency  $f_c$  and attenuates all other frequencies greater than  $f_c$  is called?

a) high pass filter

b) low pass filter

c) band elimination filter

d) band pass filter

(lviii) A filter which attenuates all frequencies below a designated cut-off frequency  $f_c$  and passes all other frequencies greater than  $f_c$  is called?

a) band elimination filter

b) band pass filter

c) low pass filter

d) high pass filter

(lix) A filter that passes all frequencies lying outside a certain range, while it attenuates all frequencies between the two designated frequencies is called?

a) high pass filter

b) band elimination filter

c) band pass filter

d) low pass filter

(lx) The Laplace transform of a function  $f(t)$  is?

a)

b)

$$\int_0^{\infty} f(t) e^{-st} dt$$

c)

$$\int_0^{\infty} f(t) e^{st} dt$$

$$\int_{-\infty}^0 f(t) e^{-st} dt$$

d) None of these