



BRAINWARE UNIVERSITY

Term End Examination 2020 - 21

Programme – Diploma in Electronics & Communication Engineering

Course Name – Electronics Instruments and Measurements

Course Code - DECE502

Semester / Year - Semester V

Time allotted : 85 Minutes

Full Marks : 70

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

(Multiple Choice Type Question)

1 x 70=70

1. (Answer any Seventy)

(i) A dynamometer wattmeter can be used for

- | | |
|-----------------------|------------------|
| a) D.C. only | b) A.C. only |
| c) both D.C. and A.C. | d) none of these |

(ii) The full range of audibility in audio frequency oscillator is

- | | |
|--------------------|--------------------|
| a) 0 to 20 Hz | b) 20 Hz to 2 kHz |
| c) 20 Hz to 20 kHz | d) 20 Hz to 20 MHz |

(iii) The frequency can be measure by

- | | |
|----------------------|----------------------|
| a) wien's bridge | b) Schering Bridge |
| c) De Sauty's Bridge | d) Anderson's Bridge |

(iv) Error of measurement =

- | | |
|--------------------------------|---------------------------|
| a) True value – Measured value | b) Precision – True value |
| c) Measured value – Precision | d) None of these |

(v) At high frequencies the capacitive reactance.

- | | |
|----------------|-----------------|
| a) is constant | b) increases |
| c) decreases | d) becomes zero |

(vi) Noise is a function of _____

- a) voltage
- b) current
- c) bandwidth
- d) frequency

(vii) The commonly used detectors in ac bridges is/are

- a) Head phones
- b) Vibration galvanometers
- c) Tuned amplifiers
- d) all

(viii) In function generator, the output waveform of integrator is

- a) Sinusoidal
- b) Square
- c) Triangular
- d) Saw-tooth

(ix) A liquid crystal display requires

- a) An AC drive
- b) A DC drive
- c) Both AC and DC drive
- d) None of these

(x) Q meter is used to measure the properties of

- a) Inductive coils
- b) Non inductive coils
- c) Capacitive coils
- d) Both (Inductive coils) and (Capacitive coils)

(xi) Ballistic galvanometer are principally used for the measurement of

- a) Current
- b) Voltage
- c) Power
- d) Electric charges

(xii) The Wien's bridge is suitable for the measurement of frequency of the range of

- a) Less than 100 Hz
- b) 100 Hz to 100 kHz
- c) 1 kHz to 100 MHz
- d) More than 100 MHz

(xiii) Schering bridges are used for the measurement of

- a) Unknown capacitance
- b) Dielectric loss
- c) Power factor
- d) All of these

(xiv) Q meter works on the principle of

- a) Series resonance
- b) Parallel resonance
- c) Both (Series resonance) and (Parallel resonance)
- d) Neither series resonance nor parallel resonance

(xv) The Ac Bridge used for the measurement of inductance is/are

- a) Maxwell's inductance bridge
- b) Hay's bridge
- c) Anderson's bridge, Owen's bridge
- d) All of These

(xvi) CRO is a _____

- a) fast x-y plotter
- b) slow x-y plotter
- c) medium x-y plotter
- d) not a plotter

(xvii) Electron gun section _____

- a) provides sharp beam
- b) provides poorly focussed beam
- c) doesn't provide any beam
- d) provides electrons only

(xviii) In CRO Control grid is given _____

- a) positive voltage
- b) negative voltage
- c) neutral voltage
- d) zero voltage

(xix) What determines light intensity in a CRT?

- a) voltage
- b) current
- c) momentum of electrons
- d) fluorescent screen

(xx) Deflection system of a CRT consists of _____

- a) 4 plates
- b) 6 plates
- c) 2 plates
- d) 8 plates

(xxi) Input signals are amplified in CRO using _____

- a) rectifier
- b) amplifier
- c) oscillator
- d) op amp

(xxii) Why is a delay line used in a CRO?

- a) to boost the signal
- b) to distort the signal
- c) to provide signal delay
- d) for stability

(xxiii) What is the problem with using more than one oscilloscopes?

- a) measuring the signal's parameters
- b) triggering
- c) supply voltage
- d) errors in reading

(xxiv) In CRO, after pre-amplification the signals are fed into

- a) an electronic switch
- b) a signal generator
- c) a rectifier
- d) a regulator

(xxv) X and Y plates of a CRO are connected to unequal voltages of equal frequency with phase shift of 90 degree. The Lissajous figure on the screen will be?

- a) Circle
- b) Straight Line
- c) Ellipse
- d) Figure of Eight

(xxvi) In Q meter, voltage across the shunt is measured by _____

- a) voltmeter
- b) multimeter
- c) thermocouple
- d) thermometer

(xxvii) Wattmeter reading has errors induced by _____

- a) resistance
- b) self-capacitance
- c) self-inductance
- d) mutual inductance

(xxviii) A.C. voltages are measured using _____

- a) oscillators and op amps
- b) rectifiers and filters
- c) resistor and capacitor
- d) inductor and resistor

(xxix) What is the effect of the capacitor on the output of Dual slope converter?

- a) no effect
- b) charging effect
- c) electrostatic effect
- d) magnetic effect

(xxx) In ramp technique Resolution depends on

- a) frequency
- b) resistance
- c) voltage
- d) current

(xxxii) A successive approximation type DVM makes use _____

- a) of a digital divider
- b) of an analog divider
- c) of an oscillator
- d) of a transducer

(xxxiii) Successive approximation type DVM is based on the principle of _____

- a) acceleration of an object
- b) weight of an object
- c) velocity of an object
- d) momentum of an object

(xxxiv) Resolution of a successive approximation type DVM is given by the relation.

- a) $R = \frac{1}{10}^n$
- b) $R = \frac{1}{10}$
- c) $R = 10^n$
- d) $R = 10$

(xxxv) Speed of a successive approximation type DVM can be improved by making use of _____

- a) electrical switches
- b) mechanical devices
- c) solid state devices
- d) transformers

(xxxv) Digital voltmeters converts _____

- a) analog to digital signal
- b) digital to analog signal
- c) current to voltage
- d) resistance to voltage

(xxxvi) In a DVM, a transducer converts _____

- a) input to proportional current
- b) input to proportional power
- c) input to proportional voltage
- d) input to proportional resistance

(xxxvii) Input range of DVM is _____

- a) 1 V to 1000 V
- b) 0.1 V to 10 V
- c) 0.01 V to 1 V
- d) 0.001 V to 0.1 V

(xxxviii) What is the effect of IC chips on DVM?

- a) increase in cost
- b) increase in power
- c) reduction in cost
- d) increase in size

(xxxix) In D.C. circuits, power is measured using _____

- a) ohmmeter and galvanometer
- b) ohmmeter and voltmeter
- c) ammeter and voltmeter
- d) ammeter and galvanometer

(xl) A dynamometer type wattmeter consists of _____

- a) only potential coil
- b) potential and current coils
- c) only current coil
- d) no coils

(xli) When the moving coil in a Dynamometer type wattmeter deflects

- a) pointer moves
- b) pointer doesn't move
- c) current flows
- d) voltage is generated

(xlii) What is the effect of capacitance on wattmeter reading?

- a) aiding the inductance
- b) opposite to that of inductance
- c) aiding the capacitance
- d) opposite to that of resistance

(xliii) Dynamometer type wattmeter has _____

- a) strong magnetic field
- b) intermediate magnetic field
- c) weak magnetic field
- d) no magnetic field

(xliv) Wattmeters are compensated for errors due to inductance by _____

- a) using a series capacitor
- b) using a parallel capacitor
- c) using a series resistance
- d) using a parallel resistance

(xlv) What is the effect of frequency on the torque of a moving system?

- a) torque is half of the frequency
- b) torque is twice the frequency
- c) torque is thrice the frequency
- d) torque is four times the frequency

(xlvi) An Oscilloscope indicates _____

- a) The peak to peak value of the voltage
- b) DC value of the voltage
- c) rms value
- d) average value

(xlvii) The disadvantage of Maxwell Bridge is?

- a) Inductance cannot be measured over a wide range
- b) Measurement is not independent of frequency
- c) Number of components is large
- d) Inductance can be measured over a wide range

(xlviii) In CRO horizontal deflection is given by _____

- a)
- b)

$X = K_x$

$X = V_x$

c) $X=1$

d)

$$X = K_x V_x$$

(xlix) Schering bridge is used for _____

- a) low voltages only
- b) low and high voltages
- c) high voltages only
- d) intermediate voltages only

(l) For phase angles close to 90° , the power factor of the Schering bridge is

a)

$$\text{p.f.} = \omega R_x$$

c) p.f. = $R_x C_x$

b)

$$\text{p.f.} = \omega C_x$$

d)

$$\text{p.f.} = \omega R_x C_x$$

(li) Quality factor is given by the expression

a)

$$Q = \frac{1}{R}$$

c)

$$Q = \frac{X}{R} C$$

b) $Q = R$

d) $Q = XR$

(lii) Bridge must be balanced for _____

- a) magnitude
- b) angle
- c) magnitude and angle
- d) power

(liii) For inductive impedances, the phase angle is _____ for Bridge balance.

- a) Positive
- b) negative

c) zero

d) exponential

(liv) For capacitive impedances, the phase angle is _____ for Bridge balance.

a) tangential

b) negative

c) positive

d) logarithmic

(lv) At very low frequencies in a AC bridge, the source is _____

a) power line

b) e.m.f

c) galvanometer

d) tuned circuit

(lvi) Tuned amplifiers can be set to _____

a) low frequencies

b) high frequencies

c) any frequency

d) audio frequencies

(lvii) In the simplest form, an AC bridge consists of _____

a) arms, source and a detector

b) arms and source

c) source and detector

d) arms and detector

(lviii) What is the frequency range for a headphone as a detector?

a) 20 Hz to 20 kHz

b) 10 kHz to 1 MHz

c) 0 MHz to 1 GHz

d) 250 Hz to 4 kHz

(lix) Tuned detectors are used in the frequency range of _____

a) 1 Hz to 100 Hz

b) 10 Hz to 100 Hz

c) 1 kHz to 100 kHz

d) 1 MHz to 100 MHz

(lx) What is applied to the two opposite junctions of a bridge circuit.

a) source of voltage

b) source of current

c) source of power

d) source of impedance

(lxi) A bridge circuit uses which method of measurement?

- a) absolute
- b) relative
- c) differential
- d) comparison

(lxii) The accuracy of a bridge depends on the _____

- a) null indicator
- b) bridge components
- c) current source
- d) voltage source

(lxiii) Q factor of a coil measured by the Q Meter is _____ the actual Q of the coil.

- a) Equal to
- b) Same but somewhat lesser than
- c) Same but somewhat higher than
- d) Not equal to

(lxiv) Relationship at balance condition between the component values of the four arms of a bridge is known as

- a) full load condition
- b) open circuit condition
- c) short circuit condition
- d) balancing condition

(lxv) Accuracy of bridge circuit depends on _____

- a) component values
- b) null detector
- c) voltage source
- d) current source

(lxvi) The bridge circuit can be used in _____

- a) high voltage circuits
- b) low power circuits
- c) control circuits
- d) digital integrated circuits

(lxvii) Commonly used D.C. bridges are _____

- a) Schering and Anderson
- b) Maxwell inductance and capacitance
- c) DeSauty and Wagner
- d) Wheatstone and Kelvin

(lxviii) Electronic voltmeter are _____

- a) measure high level signals
- b) measure low level signals
- c) measure medium level signals
- d) do not measure any signals

(lxix) Loading effect in electronic voltmeter is _____

- a) nil
- b) high
- c) low
- d) medium

(lxx) A voltmeter has a sensitivity of 1000 ohm/V reads 200 V on its 300 V scale. When connected across an unknown resistor in series with a millimeter. When the milliammeter reads 10 mA. The error due to the loading effect of the voltmeter is _____

- a) 0.0333
- b) 0.0667
- c) 0.1334
- d) 0.1367