

(Long Answer Type Questions)

5 x 6=30

7. Comparison between FET and BJT (5)
8. Explain the use of an OPAMP as summing amplifier. (5)
9. Explain the use of an OPAMP as summing amplifier. (5)
10. Differentiate between Latch And Flip-flop (5)
11. Explain operation of triac (5)
12. Explain the construction of J-K flip flop using S-R flip flop (5)
OR
Differentiate LED and LCD (5)

LIBRARY
Brainware University
Barasat, Kolkata -700125