



(ix) A 10mH inductor carries a sinusoidal current of 1 A rms at a frequency of 50hz. Calculate the average power dissipated by the inductor.

- a) 0.25 W
- b) 0 W
- c) 0.5 W
- d) none of the above

(x) What causes the depletion region?

- a) doping
- b) diffusion
- c) barrier potential
- d) ions

(xi) What is the current gain for a common-base configuration where  $I_E = 4.2$  mA and  $I_C = 4.0$  mA?

- a) 16.80
- b) 1.05
- c) 0.20
- d) 0.95

(xii) In a practical magnetic circuits, the airgap is kept

- a) very small
- b) large
- c) very large
- d) none of the above

(xiii) A half cycle average voltage of 12v is equal to what rms voltage

- a) 6v
- b) 24v
- c) 13.33v
- d) 10.5v

(xiv) Identify that an Electric circuit having nither an emf source nor an energy source is

- a) Active circuit
- b) Passive circuit
- c) Unilateral circuit
- d) bilateral circuit

(xv) Barrier potential in a PN junction is caused by


- a) Flow of drift current
- b) Diffusion of majority carriers across the junction
- c) Migration of minority carriers across the junction
- d) Thermally-generated electrons and holes

### Group-B

(Short Answer Type Questions)

3 x 5=15

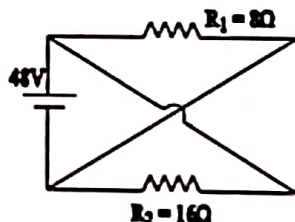
2. Describe with necessary diagram current division rule. (3)
3. Describe about the BH curve. (3)
4. Distinguish between avalanche breakdown and Zener breakdown. (3)
5. Explain the working of NPN and PNP transistor (3)
6. Calculate the current suppliiued by the battery in the given circuit. (3)



OR

Evaluate the current through each resistors,


(3)

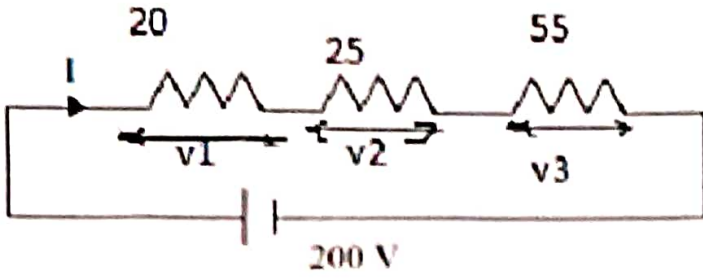

**Group-C**  
(Long Answer Type Questions)

5 x 6=30

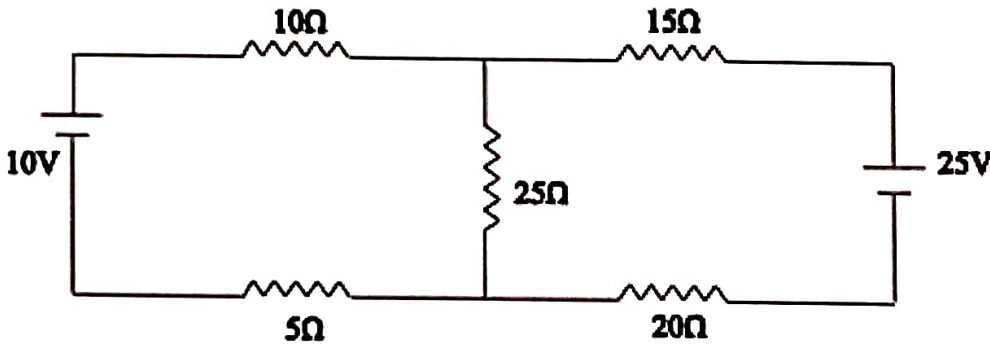7. Describe the working principle of transformer. (5)
8. Describe and prove that input and output power of transformer is same. (5)
9. Explain the center-tap Full wave rectifier with a neat diagram. (5)
10. Draw and explain the input and output characteristics of a transistor in CC configuration. (5)
11. Support by a phasor diagram show that the sum of the three-phase balanced currents is zero (5)
12. Calculate the branch current using 15 ohm resistance. (5)



OR

Evaluate the value of R in the circuit

(5)

