



BRAINWARE UNIVERSITY

Term End Examination 2023-2024

Programme – Dip.EE-2021

Course Name – Basic Electronics

Course Code - DEE303

(Semester III)

LIBRARY
Brainware University
Barasat, Kolkata - 700125

Time : 2:30 Hours

Full Marks : 60

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

(Multiple Choice Type Question)

1 x 15=15

1. Choose the correct alternative from the following :


- (i) Choose the base current amplification factor β is given by
- a) I_C/I_B
 - b) I_B/I_C
 - c) I_E/I_B
 - d) I_B/I_E
- (ii) Tell, the doping of the emitter region of a transistor is
- a) Larger than that of collector region
 - b) Less than that of collector region
 - c) Equal to that of collector region
 - d) None of these
- (iii) Select the option for which semiconductor diode is used
- a) oscillator
 - b) rectifier
 - c) amplifier
 - d) None of these
- (iv) Cite the acceptor impurities
- a) Generate electrons
 - b) Generate holes
 - c) Generate hole and electrons
 - d) All of these
- (v) If FET employed in cut-off, the depletion layers are
- a) Touching each other
 - b) Close together
 - c) Far apart
 - d) None of these
- (vi) A FET produce output due to
- a) Majority carriers only
 - b) Minority carriers
 - c) Positive and negative ions
 - d) Positively charged ions
- (vii) Identify the option which represent p-n junction diode's dynamic conductance is directly proportional to
- a) The applied voltage
 - b) The temperature
 - c) Its current
 - d) None of these
- (viii) During reverse bias, a small current develops which is named as
- a) Forward current
 - b) Reverse current
 - c) Reverse saturation current
 - d) Active current
- (ix) Identify which of the following is true in construction of a transistor?

- a) The collector dissipates less power
 c) The collector is made physically larger than the emitter region
- (x) Identify the Universal Gate
 a) AND
 c) NAND
- (xi) Identify the terminal of JFET
 a) anode, cathode, grid
 b) source, gate, drain
- (xii) Choose cut off voltage if the pinch off voltage of JFET is 5V.
 a) 2.5 V
 c) 7.5 V
- (xiii) Relate between alpha and beta
 a) $\beta = 1 + (\alpha - 1)$
 c) $\alpha = \beta / (\beta - 1)$
- (xiv) Identify active region of a transistor
 a) Both emitter and collector junctions are reverse biased
 c) Emitter junction is forward biased and collector junction is reverse biased
- (xv) For a p-n-p transistor in CE mode, $\beta = 100$, then identify the value of α of the transistor
 a) 0.99
 c) 9.9
- b) The emitter supplies minority carriers
 d) The collector collects minority charge carriers
- b) OR
 d) XOR
- b) emitter, base, collector
 d) none of them
- b) 5 V
 d) 0 V
- b) $\alpha = \beta / (\beta + 1)$
 d) $\beta = 1 / (1 - \alpha)$
- b) Both emitter and collector junctions are reverse biased
 d) None of these
- b) 0.099
 d) 99

Group-B
 (Short Answer Type Questions)

3 x 5 = 15

 2. Explain feedback and why it is required. (3)
 3. Develop the gain of a system with negative feedback. (3)
 4. Explain different series feedback amplifier topologies. (3)
 5. Explain different shunt feedback amplifier topologies. (3)



Write the transfer function (input/output equation) for an operational amplifier with an open-loop voltage gain of 100,000, and the inverting input connected to a voltage divider on its output terminal (so the inverting input receives exactly one-half the output voltage). In other words, develop an equation describing the output voltage of this op-amp (V_{out}) for any given input voltage at the non-inverting input (V_{in}):

OR

(3)

$$V_o = \frac{R_3}{R_1 + R_3} \frac{R_2 + R_4}{R_2} V_1 - \frac{R_4}{R_2} V_2$$


Propose how many op-amps are required to implement this equation?

Group-C
(Long Answer Type Questions)

5 x 6 = 30

7. Explain the functionality of 3:8 decoder (5)
8. A JFET has $I_{DSS} = 12 \text{ mA}$ and $V_{GS(off)} = -4\text{V}$. Determine the minimum value of V_{DD} required to put the device in the constant current region of operation. (5)

9. (5)

 

Dr. Pratik Kumar
Mob: 9896111111

Evaluate the output voltage V_o if $V_1 = -V_2 = 300 \text{ mV}$.

10. Describe the various methods used for transistor biasing. (5)
11. Explain base resistor method of transistor biasing. (5)
12. Design an non - inverting amplifier and derive its gain. (5)

OR

Design a subtractor circuit using op-amp. (5)
