



BRAINWARE UNIVERSITY

Term End Examination 2023 Programme – Dip.EE-2019/Dip.EE-2021 Course Name – Applied and Digital Electronics Course Code - DEE404 (Semester IV)

		RAR	٧ .	
Deal			MARKET SEA	ry
Bra	M K	olkat	-700	125
Bar a	PO.1			

Full Marks: 60

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

1.	(Mu Choose the correct alternative from	ultiple Choice Type Question) m the following:	1 x 15=15
(i) Any signed negative binary number is identified by its			
(ii)	a) MSB c) Byte	b) LSB d) Nibble distinct values can be represented is know	n as
	a) Bit c) Word	b) Byte d) Nibble term, calculate how many combination will	
(iv)	a) 0c) 2A variable on its own or in its cor	b) 1 d) 3 nplemented form is written as a	
	a) Product Term c) Sum Term On multiplication of (10.10) and	b) Literal	_
	a) 101.001 c) 11.001	b) 10.101 d) 110.0011 of the corresponding Minterm with its	literal
	a) Terms c) Numbers) 1's complement of 1011101 is	b) Words d) Nibble	
	a) 101110 c) 100010 i) There are Minte	b) 1001101 d) 1100101 erms for 3 variables (a, b, c)	
	a) 0 c) 8	b) 2 d) 1	

LIBRARY Brainware University Barasat, Kolkata -760125

(ix) All input of NOR as low produces result as	SSERIE Anni Participa de Angliar Esta Assanta Anni Anni Anni Anni Anni Anni Anni Ann	
a) Low	b) Mid	
c) High	d) Floating	
 (x) RTL constructs of a common emitter stage base and the input voltage source. 	with a connected between the	
a) collector	b) base resistor	
c) capacitor	d) inductor	
(xi) Select the input given to "R" when SR flip -	flop is converted to JK flip – flop?	
CS100 C) LO	b) K.Q'	
C2. 50 C) TO 10 N	d) J.Q'	
(xii) Which of the following options represent the	ne correct reduction of XYZ + XYZ ?	
a) 0	b) YZ	
c) X + X	d) 2YZ	
(xiii) Select which of these pins will allow to acti-	vate and deactivate a multiplexer?	
a) Enable pin	b) Selection pin	
c) Logic pin	d) Preset pin	
(xiv) Calculate how many entries will be in the tr	uth table of a 4-input NAND gate?	
a) 6	b) 8	
c) 32	d) 16	
(xv) Show the Division of the binary number: 11	1001 ÷ 1101 and find the reminder	
a) 1010	b) 110	
c) 101	d) 11	
	roup-B	2 5 45
(Short Answe	er Type Questions)	3 x 5=15
2. What is priority encoder? Give a brief demonst	tration on Encoder.	(3)
3. What is Master slave J-K flip flop? Explain race		(3)
4. Demonstration on D Flip Flop.		(3)
5. Explain fan in and fan out.		(3)
6. Analyze the two hazards that can be there in a	combinational circuit?	(3)
	OR	
Explain how to avoid static hazards in a combin hazards)?	national circuit(single variable change	(3)
G	roup-C	
	r Type Questions)	5 x 6=30
(2011)		
- 1) III NAND gate ii) Establish the action	of NAND gate as Universal gate.	(5)
7. i) Illustrate NAND gate. ii) Establish the action of NAND gate as Universal gate. 8. Represent a full-subtractor using fewer (i) NAND gates, (ii) NOR gates.		(5)
	UP/DOWN counter with JK flip flop.	(5)
 Explain the design of a MOD 14 asynchronous Illustrate NOR gate and demonstrate the action 	n of NOR gate as Universal gate.	(5)
11. Compare the performance of binary serial and	parallel adders.	(5)
12. Design a SR Flip Flop using JK Flip Flop with su	itable explanation.	(5)
	OR	
(a) Write down the applications of four basic fl		(5)
obtained by using gates only. Describe its action	on. Give its symbol and truth table	
Obtained by doing Bates only, 2 contract to		