



BRAINWARE UNIVERSITY

Term End Examination 2023
Programme – B.Tech.(ECE)-2019
Course Name – Analog Circuits
Course Code - PCC-EC402
(Semester IV)

LIBRARY
Brainware University
Barasat, Kolkata -700125

BRUN
UNIVERSITY
LIBRARY
BARASAT - KOLKATA - 700125

Full Marks : 60

Time : 2:30 Hours

[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

(Multiple Choice Type Question)

1 x 15=15

1. Choose the correct alternative from the following :

- (i) If the positive terminal of the battery is connected to the anode of the diode, then it is known as
 - a) Forward biased
 - b) Reverse biased
 - c) Equilibrium
 - d) Schottky barrier
- (ii) When a forward bias is applied to a diode, the electrons enter to which region of the diode?
 - a) P-region
 - b) N-region
 - c) P-n junction
 - d) Metal side
- (iii) The current in the diode is contributed by
 - a) majority carriers only
 - b) minority carriers only
 - c) both majority and minority carriers
 - d) none of these
- (iv) Which of the following is true about the resistance of a Zener diode?
 - a) It has an incremental resistance
 - b) It has dynamic resistance
 - c) The value of the resistance is the inverse of the slope of the i-v characteristics of the Zener diode
 - d) All of these
- (v) Which of the following can be used in series with a Zener diode so that combination has almost zero temperature coefficient?
 - a) Diode
 - b) Resistor
 - c) Transistor
 - d) MOSFET
- (vi) In Zener diode, for currents greater than the knee current, the V-I curve is almost
 - a) Almost a straight line parallel to y-axis
 - b) Almost a straight line parallel to x-axis
 - c) Equally inclined to both the axes with a positive slope
 - d) Equally inclined to both the axes with a negative slope
- (vii) With both bases grounded, the only offset that produces an error is the

- a) Input offset current
 c) Input offset voltage
- b) Input bias current
 d) Beta
- (viii) What usually controls the open-loop cutoff frequency of an op amp?
 a) Stray-wiring capacitance
 c) Collector-base capacitance
- b) Base-emitter capacitance
 d) Compensating capacitance
- (ix) What will be the voltage drop across the source resistance of differential amplifier when connected in open loop configuration?
 a) Zero
 c) One
- b) Infinity
 d) Greater than one
- (x) Determine the output voltage for the non-inverting amplifier input voltage $37\mu\text{Vpp}$ sine wave. Assume that the output is a 741.
 a) -7.44 Vpp sine wave
 c) 7.4Vpp sine wave
- b) 74 Vpp sine wave
 d) 0.7 Vpp sine wave
- (xi) What happens if any positive input signal is applied to open-loop configuration?
 a) Output reaches saturation level
 c) Output will be a sine waveform
- b) Output voltage swing's peak to peak
 d) Output will be a non-sinusoidal waveform
- (xii) Which of the following is a combination of inverting and non-inverting amplifier?
 a) Differential amplifier with one op-amp
 c) Differential amplifier with three op-amps
- b) Differential amplifier with two op-amps
 d) Differential amplifier with four op-amps
- (xiii) Compute the output voltage if the input voltage is reduced to zero in differential amplifier with one op-amp?
 a) Inverted Voltage
 c) Amplified inverted voltage
- b) Same as the input voltage
 d) Cannot be determined
- (xiv) Which of the following is a method to model a diode's forward characteristics?
 a) Iteration method
 c) Constant-voltage drop model
- b) Graphical method
 d) All of these
- (xv) How many junctions does a diode consist of?
 a) 0
 c) 2
- b) 1
 d) 3

Group-B

(Short Answer Type Questions)

3 x 5=15

2. Draw the necessary circuit diagram and express the expression of voltage gain from an OPAMP being used as a non-inverting amplifier. (3)
3. Draw the circuit diagram of a differential amplifier using an OPAMP and express an expression for the output voltage. (3)
4. What is the slew rate? Explain virtual ground concept of an Op-Amp. (3)
5. Explain the operation of a phase-shift oscillator with the help of a circuit diagram. (3)
6. Develop the theory of action of an OPAMP as an integrator. Draw the circuit diagram of a practical integrator. (3)

OR

Explain the use of an OPAMP as a non-inverting amplifier. (3)

Group-C

(Long Answer Type Questions)

5 x 6=30

7. Explain Hartly oscillator and derive the equation for oscillation? (5)
8. Draw the symbol of OPAMP and explain the characteristics of ideal OPAMP. (5)
9. Write a short note on virtual ground. (5)
10. Explain the use of an OPAMP as a summing amplifier. (5)

11. Develop the use of an OPAMP as a differential amplifier. (5)
12. Explain the action of Zener diodes, illustrating both avalanche breakdown and Zener break down. (5)

OR

With respect to CB output characteristics of a transistor, explain the active, saturation and the cut-off region (5)

LIBRARY
Brainware University
Barasat, Kolkata -700125

Brainware University
Barasat, Kolkata -700125
25/10/21