



# BRAINWARE UNIVERSITY

Term End Examination 2021 - 22

Programme – Diploma in Electronics & Communication Engineering

Course Name – Industrial Electronics I

Course Code - DECE504

( Semester V )

Time : 1 Hr.15 Min.

Full Marks : 60

[The figure in the margin indicates full marks.]

## Group-A

(Multiple Choice Type Question)

1 x 60=60

Choose the correct alternative from the following :

- (1) Which of the following devices does not belong to the transistor family?
 

a) IGBT	b) MOSFET
c) GTO	d) BJT
- (2) In a power transistor, \_\_\_\_ is the controlled parameter.
 

a) VCE	b) VBE
c) IB	d) IC
- (3) In a power transistor, \_\_\_\_\_ is the controlling parameter.
 

a) VCE	b) VBE
c) IB	d) IC
- (4) For a power transistor, if the base current IB is increased keeping VCE constant, then
 

a) IC increases	b) IC decreases
c) IC remains constant	d) none of these
- (5) The value of  $\beta$  is given by the expression
 

a) $IC/IB$	b) $IC/IE$
c) $IE/IC$	d) $IE/IB$
- (6) A power BJT is used as a power control switch by biasing it in the cut off region (off state) or in the saturation region (on state). In the on state
 

a) both the base-emitter & base-collector junctions are forward biased	b) the base-emitter junction is reverse biased, and the base collector junction is forward biased
c) the base-emitter junction is forward biased, and the base collector junction is reversed biased	d) both the base-collector & the base-emitter junctions are reversed biased

(7) For a power transistor, if the forward current gain  $\alpha = 0.97$ , then  $\beta$

- a) 0.03  
b) 2.03  
c) 49.24  
d) 32.33

LIBRARY  
Brainware University  
Barasat, Kolkata - 700125

(8) For a power transistor, which of the following relations is true?

- a)  $I_e > I_c > I_b$   
b)  $I_b > I_c > I_e$   
c)  $I_c > I_e > I_b$   
d)  $I_e = I_b$

(9) The instantaneous power loss during the delay time of a transistor is given by

- a)  $I_c V_{ce}$   
b)  $I_b V_{be}$   
c)  $I_c V_{be}$   
d)  $I_b V_{ce}$

(10) A 1mv of i/p gives an output of 1V, the voltage gain as such would be

- a) 0.001  
b) 0.0001  
c) 1000  
d) 100

(11) Which of the following relations is true for a BJT?

- a)  $I_c \approx I_e$   
b)  $I_b \approx I_c$   
c)  $I_e \approx I_b$   
d)  $I_b \approx I_e \approx I_c$

(12) Choose the correct statement

- a) A transistor will remain on as long the the base current is applied  
b) A transistor remains on after a high to low pulse is applied at the base  
c) A transistor will remain on as long the the collector current is applied  
d) A transistor remains on after a high to low pulse is applied at the collector

(13) A thyristor (SCR) is a

- a) P-N-P device  
b) N-P-N device  
c) P-N-P-N device  
d) P-N device

(14) Choose the false statement.

- a) SCR is a bidirectional device  
b) SCR is a controlled device  
c) In SCR the gate is the controlling terminal  
d) SCR are used for high-power applications 12 80 $\mu$ s

(15) The static V-I curve for the SCR is plotted for

- a)  $I_a$  (anode current) vs  $I_g$  (gate current),  $V_a$  (anode - cathode voltage) as a parameter  
b)  $I_a$  vs  $V_a$  with  $I_g$  as a parameter  
c)  $V_a$  vs  $I_g$  with  $I_a$  as a parameter  
d)  $I_g$  vs  $V_g$  with  $I_a$  as a parameter

(16) For an SCR in the reverse blocking mode, (practically)

- a) leakage current does not flow  
b) leakage current flows from anode to cathode  
c) leakage current flows from cathode to anode  
d) leakage current flows from gate to anode

(17) For an SCR in the forward blocking mode (practically)

- a) leakage current does not flow  
b) leakage current flows from anode to cathode  
c) leakage current flows from cathode to anode  
d) leakage current flows from gate to anode

(18) For a forward conducting SCR device, as the forward anode to cathode voltage is increased

- a) the device turns on at higher values of gate c  
b) the device turns on at lower values of gate c



- urrent  
c) the forward impedance of the device goes on increasing
- urrent  
d) the forward impedance of the device goes on decreasing
- (19) A thyristor can be bought from the forward conduction mode to forward blocking mode by
- a) the dv/dt triggering method  
b) applying a negative gate signal  
c) applying a positive gate signal  
d) applying a reverse voltage across anode-cathode terminals
- (20) Usually the forward voltage triggering method is not used to turn-on the SCR because
- a) it increases losses  
b) it causes noise production  
c) it may damage the junction & destroy the device  
d) relatively it's an inefficient method
- (21) The forward break over voltage is maximum when
- a) Gate current =  $\infty$   
b) Gate current = 0  
c) Gate current =  $-\infty$   
d) It is independent of gate current
- (22) The value of anode current required to maintain the conduction of an SCR even though the gate signal is removed is called as the
- a) holding current  
b) latching current  
c) switching current  
d) peak anode current
- (23) \_\_\_\_\_ are semiconductor thyristor devices which can be turned-on by light of appropriate wavelengths.
- a) LGTOs  
b) LASERs  
c) MASERs  
d) LASCERs
- (24) During the transition time or turn-on time
- a) The forward anode voltage decreases from 100% to 10% & the anode current also decreases from 90% to 10% of the initial value  
b) The forward anode voltage increases from 10% to 90% & the anode current also increases from 10% to 90% of the initial value  
c) The forward anode voltage decreases from 100% to 10% & the anode current increases from 10% to 90% of the initial value  
d) The forward anode voltage increases from 10% to 90% & the anode current decreases from 90% to 10% of the initial value
- (25) For an SCR the total turn-on time consists of i) Delay time ii) Rise time and iii) Spread time During the delay time the
- a) anode current flows only near the gate  
b) anode current rises from zero to very high value  
c) losses are maximum  
d) anode to cathode voltage is zero
- (26) For an SCR the total turn-on time consists of i) Delay time ii) Rise time and iii) Spread time During the rise time the
- a) anode current flows only near the gate  
b) anode current rises from zero to very high value  
c) losses are maximum  
d) anode to cathode voltage is zero
- (27) For an SCR the total turn-on time consists of i) Delay time ii) Rise time and the iii) Spread time The spread time interval depends upon
- a) the value of gate current  
b) junction temperature  
c) area of the cathode  
d) area of the anode



(28) To avoid commutation failure

- a) circuit turn-off time must be greater than the thyristor turn-off time
- b) circuit turn-off time must be lesser than the thyristor turn-off time
- c) circuit turn-off time must be equal to the thyristor turn-off time
- d) none of these

LIBRARY  
Bafware University  
Berasat, Kelantan - 700125

(29) The area under the curve of the gate characteristics of thyristor gives the

- a) total average gate current
- b) total average gate voltage
- c) total average gate impedance
- d) total average gate power dissipation

(30) A tangent drawn from the Y-axis to the  $P_{avg}$  on the gate characteristics gives the value of the

- a) maximum value of gate-source resistance
- b) minimum value of gate-source resistance
- c) maximum value of gate-source power
- d) minimum value of gate-source power

(31) Higher the magnitude of the gate pulse

- a) lesser is the time required to inject the charges
- b) greater is the time required to inject the charges
- c) greater is the value of anode current
- d) lesser is the value of anode current

(32) For an SCR, the gate-cathode characteristic has a slope of 130. The gate power dissipation is 0.5 watts. Find  $I_g$

- a) 0.62 A
- b) 620 mA
- c) 62 mA
- d) 6.2 mA

(33) Latching current for an SCR is 100 mA, DC source of 200 V is also connected from the SCR to the L load. Compute the minimum width of the gate pulse required to turn on the device. Take  $L = 0.2$  H.

- a) 50 micro-sec
- b) 100 micro-sec
- c) 150 micro-sec
- d) 200 micro-sec

(34) From the two transistor ( $T_1$  &  $T_2$ ) analogy of SCR, the total anode current of SCR is \_\_\_\_\_ in the equivalent circuit.

- a) the sum of both the base currents
- b) the sum of both the collector current
- c) the sum of base current of  $T_1$  & collector current of  $T_2$
- d) the sum of base current of  $T_2$  & collector current of  $T_1$

(35) Latching current for an SCR is 100 mA, a dc source of 200 V is also connected to the SCR which is supplying an R-L load. Compute the minimum width of the gate pulse required to turn on the device. Take  $L = 0.2$  H &  $R = 20$  ohm both in series.

- a) 62.7 micro-sec
- b) 100.5 micro-sec
- c) 56.9 micro-sec
- d) 81 micro-sec

(36) A fully controlled converter uses

- a) diodes only
- b) thyristors only
- c) both diodes and thyristors
- d) none of these

(37) A single phase full controlled bridge converter (B-2) uses

- a) 4 SCRs and 2 diodes
- b) 4 SCRs
- c) 6 SCRs
- d) 4 SCRs and 2 diodes

(38) In a three-phase half wave rectifier usually, the primary side of the transformer is delta connected because

- a) it has no neutral connection
- b) we can get greater output voltage
- c) it provides a path for the triplen harmonics
- d) it provides better temperature stability

(39) In a three-phase half wave diode rectifier, if  $V_{mp}$  is the maximum phase voltage, then the output voltage on a R load varies from

- a) 0 to  $V_{mp}$   
c)  $V_{mp}$  to  $3V_{mp}$
- b)  $0.5 V_{mp}$  to  $V_{mp}$   
d)  $-V_{mp}$  to  $V_{mp}$
- (40) In a three-phase half wave 6-pulse mid-point type diode rectifier, each diode conducts for  
or  
a)  $120^\circ$   
c)  $90^\circ$   
b)  $60^\circ$   
d)  $180^\circ$
- (41) A step-down delta-star transformer, with per-phase turns ratio of 5 is fed from a 3-phase  $1100\text{ V}$ ,  $50\text{ Hz}$  source. The secondary of this transformer is connected through a 3-phase type rectifier, which is feeding an R load. Find the average value of output voltage.  
a)  $220\text{ V}$   
c)  $650.08\text{ V}$   
b)  $257\text{ V}$   
d)  $206\text{ V}$
- (42) For a 3-phase 6-pulse diode rectifier, has  $V_{ml}$  as the maximum line voltage value on R load. The peak current through each diode is  
a)  $V_{ml}/2R$   
c)  $V_{ml}/R$   
b)  $2V_{ml}/R$   
d) Insufficient Data
- (43) A 3-phase bridge rectifier charges a  $240\text{ V}$  battery. The rectifier is given a 3-phase,  $230\text{ V}$  supply. The current limiting resistance in series with the battery is of  $8\text{ ohm}$ . Find the average value of battery charging current.  
a)  $12.56\text{ A}$   
c)  $9.69\text{ A}$   
b)  $8.82\text{ A}$   
d)  $6.54\text{ A}$
- (44) For a single phase, full bridge, diode rectifier excited from a  $230\text{ V}$ ,  $50\text{ Hz}$  source. With  $R = 10\text{ ohm}$  & the inductance(L) large enough to maintain continuous conduction, the average and rms values of diode currents will be  
a)  $7.85\text{ A}$ ,  $8\text{ A}$   
c)  $10.35\text{ A}$ ,  $14.6\text{ A}$   
b)  $10.35\text{ A}$ ,  $7.85\text{ A}$   
d)  $8\text{ A}$ ,  $8\text{ A}$
- (45) The rectification efficiency for B-2 type & M-2 type full wave diode rectifiers are \_\_\_\_\_ & \_\_\_\_\_ respectively.  
a)  $8/\pi$  &  $4/\pi$   
c)  $8/\pi$  &  $8/\pi$   
b)  $4/\pi$  &  $8/\pi$   
d)  $4/\pi$  &  $4/\pi$
- (46) SPMS are based on the \_\_\_\_\_ principle.  
a) Phase control  
c) Chopper  
b) Integral control  
d) MOSFET
- (47) \_\_\_\_\_ is used for critical loads where temporary power failure can cause a great deal of inconvenience.  
a) SMPS  
c) MPS  
b) UPS  
d) RCCB
- (48) To make a signal diode suitable for high current & high voltage carrying applications with minimum losses, \_\_\_\_\_  
a) a lightly doped n layer is grown between the two p & n layers  
c) a lightly doped p layer is grown between the two p & n layers  
b) a heavily doped n layer is grown between the two p & n layers  
d) a heavily doped p layer is grown between the two p & n layers
- (49) The V-I Characteristics of the diode lie in the



- a) 1st & 2nd quadrant  
 c) 1st & 4th quadrant
- (50) A diode is said to be reversed biased when the  
 a) cathode is positive with respect to the anode  
 c) cathode is negative with respect to the anode
- (51) The peak inverse current  $I_P$  for a power diode is given by the expression  
 a)  $I_P = t \, di/dt$   
 c)  $I_P = t * di/dt$
- b) 1st & 3rd quadrant  
 d) Only in the 1st quadrant
- b) anode is positive with respect to the cathode  
 d) both cathode and anode are negative
- b)  $I_P = t * \log i$   
 d)  $I_P = t * \int t * i \, dt$
- (52) If  $V$  &  $I$  are the forward voltage & current respectively, then the power loss across the diode would be  
 a)  $V/I$   
 c)  $I^2 V$
- b)  $V^2 I^2$   
 d)  $VI$
- (53) Even after the forward current reduces to zero value, a practical diode continues to conduct in the reverse direction for a while due to the  
 a) resistance of the diode  
 c) stored charges in the depletion region
- b) high junction temperature  
 d) none of these
- (54) In an AC-DC converter, a diode might be used as a  
 a) voltage source  
 c) freewheeling Diode
- b) phase angle controller  
 d) filter
- (55) When the p-n junction diode is reversed biased, the width of the depletion region \_\_\_\_\_  
 \_\_\_\_\_  
 a) increases  
 c) remains Constant
- b) decreases  
 d) none of these
- (56) A triac can be considered as:  
 a) Two SCRs connected in anti-parallel with a common gate  
 c) Two SCRs connected in parallel with a common gate
- b) Two transistors corrected in antiparallel  
 d) Two SCRs connected in parallel with two gates
- (57) A triac is semiconductor device acting  
 a) As a diode in the forward direction and SCR in the reverse direction  
 c) As diode in both the directions
- b) As an SCR in both the directions  
 d) As an SCR in one direction and diode in the other direction
- (58) Auxiliary commutation is also known as  
 a) Class A commutation  
 c) Class D commutation
- b) Class C commutation  
 d) None of these
- (59) In the equilibrium state, the barrier potential across a unbiased silicon diode is \_\_\_\_\_  
 \_\_\_\_\_  
 a) 0.3 V  
 c) 1.3 V
- b) 0.7 V  
 d) 0 V
- (60) IGBT possess  
 a) low input impedance  
 c) high on-state resistance
- b) high input impedance  
 d) second breakdown problems