



BRAINWARE UNIVERSITY

Term End Examination 2023-2024 Programme – Dip.EE-2021 Course Name – Control of Electrical Machine Course Code - DEE604C (Semester VI)

Full Marks: 60

Time: 2:30 Hours


[The figure in the margin indicates full marks. Candidates are required to give their answers in their own words as far as practicable.]

Group-A

(Multiple Choice Type Question)

1 x 15=15

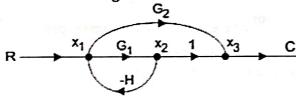- 1. Choose the correct alternative from the following:
- (i) Use mason's gain formula to calculate the transfer function of given figure:




a) $G1/(1+G_2H)$

b) $G_1+G_2/(1+G_1H)$

c) G₁G₂/1-G₁H

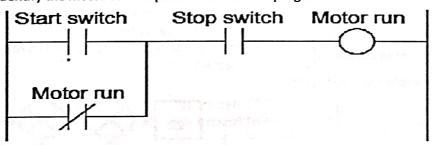- d) $G_1+G_2/(1-G_1H)$
- (ii) Identify the motor control problem in this PLC program



a) coil

b) seal in contact

c) start cotact

- d) stop contact
- (iii) Select a node that have only outgoing branches
 - a) Input node

b) Output node


c) Incoming node

- d) Outgoing node
- (iv) Select the advantage of using free wheeling diode in half controlled bridge converter is that
 - a) There is always a path for the dc current independent of the ac line
- b) There is always a path for the ac current independent of the ac line

1	c) There is always a path for the dc current dependent of the ac line	•	There is always a path for the ac current independent of the ac line
(v) List out one from the following which is not a manually operated switch.			
	a) Thumbwheel switch		Rotary selector switch
(vi	c) Crossbar switch) A relay working is associated	u)	Toggle switch
(**,	a) By using a resistor to change the current		By using an electromagnet to activate or deactivate a switch or circuit
(vii)	c) By using a semiconductor technology Regenerative feedback associated with		By using a mechanical switch
	a) positive	b)	negative
	c) oscillation	d)	step
(viii)	As a result of introduction of negative feedback in decrease	dent	ify of the following will not
	a) bandwidth	b)	oveall gain
	c) noise	d)	instability
(ix)	Identify the main component of a relay		
	a) capacitor	•	diode
6.3	c) contacts		coil
(x)	Tell that the speed of a DC shunt motor can be increased by		
	a) Increasing the resistance in armature circuit		Increasing the resistance in field circuit
	c) Reducing the resistance in the field circuit	4	Reducing the resistance in the armature circuit
(xi)	xi) Identify which of the following is the best braking method?		
	a) Friction	b)	Electromechanical action
	c) Eddy-currents		Electric braking
	Choose the main difference between online and of	ne PLC programming is	
	 a) whether the programming pc has internet connectivity 	b) ,	where the edited program resides
	 c) whether the PLC is running or stopped Identify that the capability of convention relay sys that of the PLCs. 	d) t stem	the type of program used as for complex operations is
á	a) excellent than	b) ı	poor than
(c) as good as		unpredictable as
xiv)	Identify which of the statement is correct for the	sign	al flow graph.
a	They apply to linear systems		The equation obtained may or may not be in the form of cause or effect
C	c) Arrows are not important in the graph	d) ⁻	They cannot be converted back to block diagram
xv) F	Regenerative feedback implies feedback with		
а) Oscillations	b) 9	Step input
) Negative sign		Positive sign
		, .	
Group-B			
(Short Answer Type Questions) 3 x 5=15			
			5 N 5-13

(3)

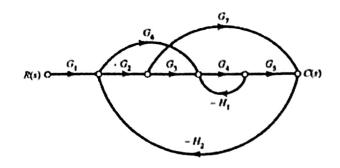2. Calculate the overall transfer function for the given signal flow graph.



- 3. State the advantages of closed-loop control system over open-loop control system.

 4. List out the main features of MCB.

 5. Identify the differences between Contactor and MCB.

 (3)

 (3)
- 5. Identify the differences between Contactor and MCB.

 (3)

 (3)

6. Write advantages and disadvantages of automatic star delta starter.

OR


Illustrate the operation ON-OFF motor control circuit with necessary diagram.

Group-C
(Long Answer Type Questions) 5 x 6=30


- 7. Explain the function of voltage operated overload relay. (5)
- 8. Describe the working of definite time acceleration starter

 9. Differentiate between Fuse and MCB.

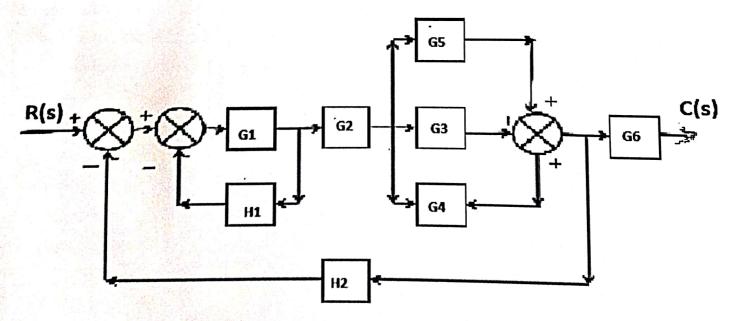 (5)
- 10. Evaluate the overall gain of the given graph. (5)
 - A B 1 1 1 V
- 11. Explain the main function of each of the major components of a PLC. (5)
- 12. Derive the transfer function. (5)



Derive the transfer function of

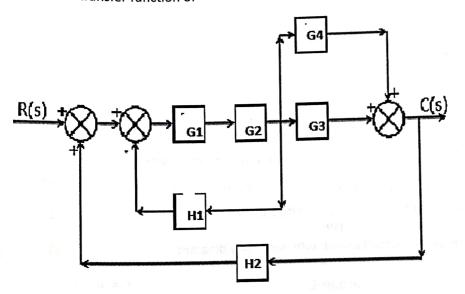

*